

Single Electron Tunneling Junctions

Paul Riechers

Modeling an isolated SETJ

1092 T. Yang & L. O. Chua

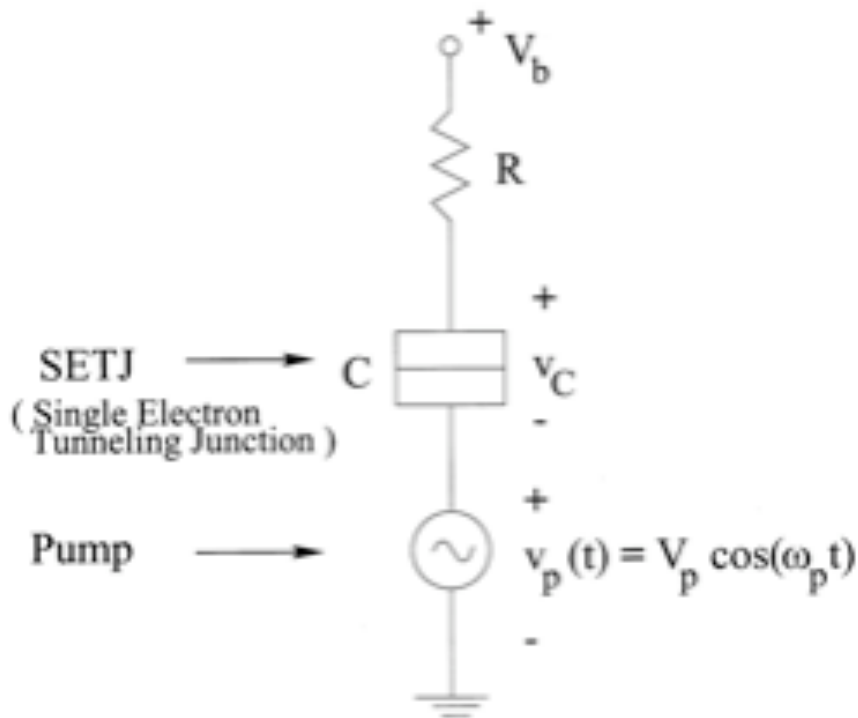


Fig. 1. An isolated driven single-electron tunneling junction circuit.


$$\frac{dv_C(t)}{dt} = \frac{1}{RC} (V_b - v_C(t) - V_p \cos(\omega_p t)), \quad \text{if } |v_C(t)| < V_T,$$


$$\Delta v_C(t_i) \triangleq v_C(t_i^+) - v_C(t_i) = \begin{cases} -2V_T, & v_C(t_i) \geq V_T, \\ 2V_T, & v_C(t_i) \leq -V_T, \end{cases}$$

$$\frac{d\theta}{dt} = -\frac{\gamma}{\pi} \theta + \gamma(a - b \cos t), \quad t \neq \tau_i,$$


$$\Delta\theta(\tau_i) = -2\pi, \quad t = \tau_i, \\ |\theta(0)| < \pi,$$

Stages of Tunneling in SETJ

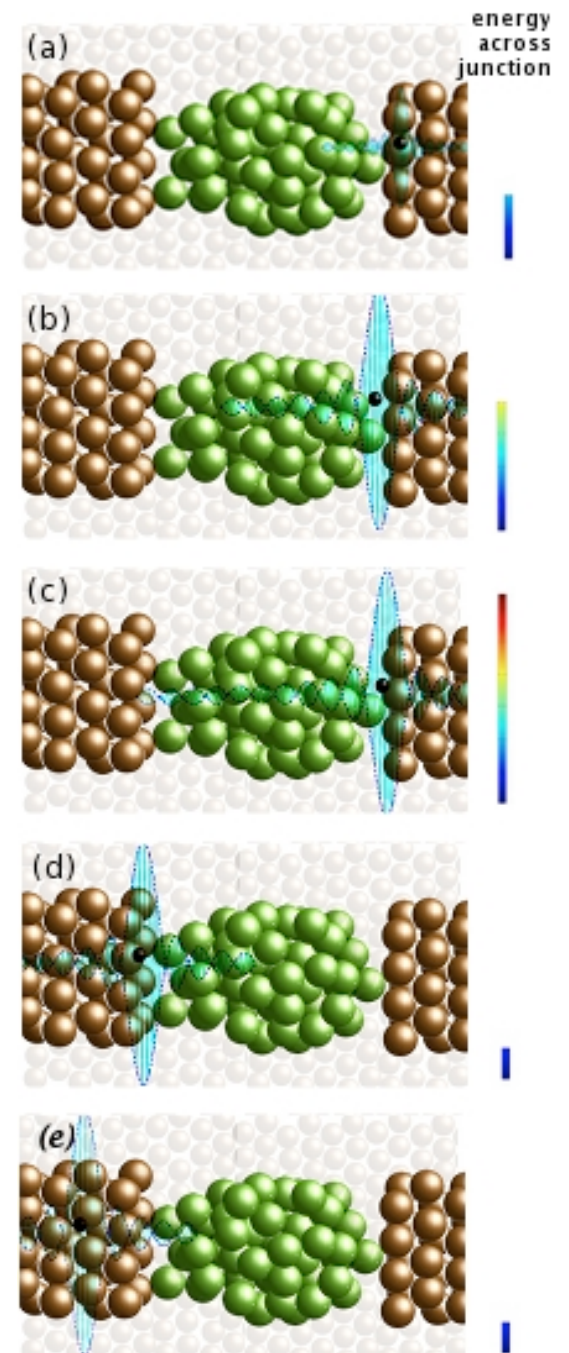

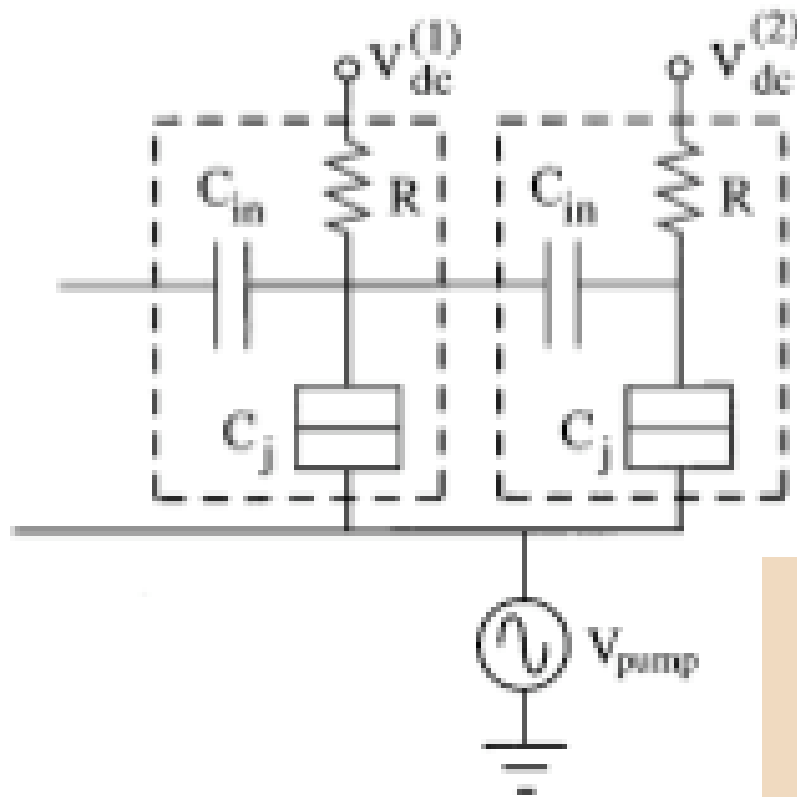

From isolated SETJ
circuits to arrays

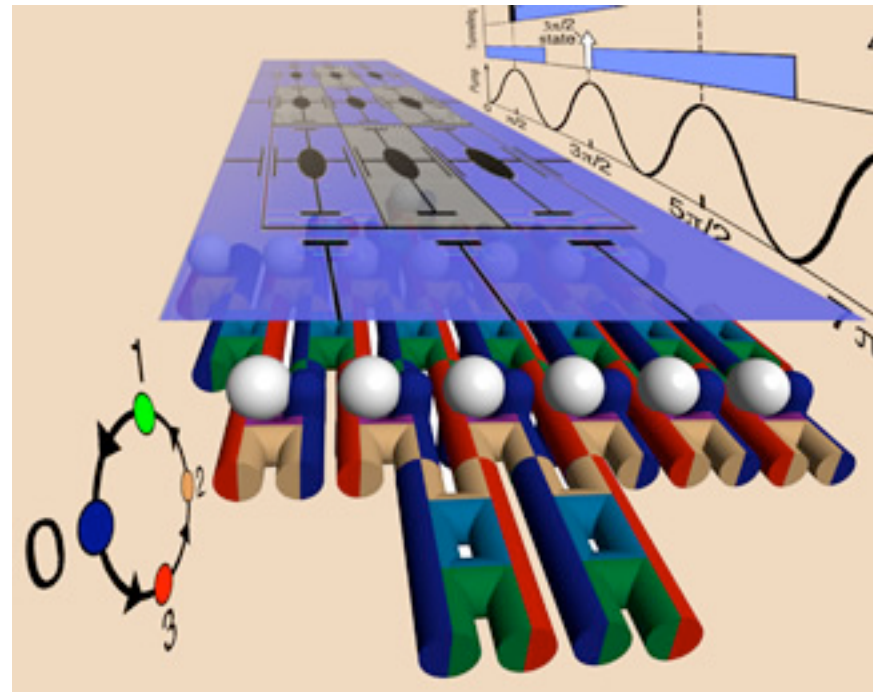

Now, back to the isolated SETJ circuit...

1092 T. Yang & L. O. Chua

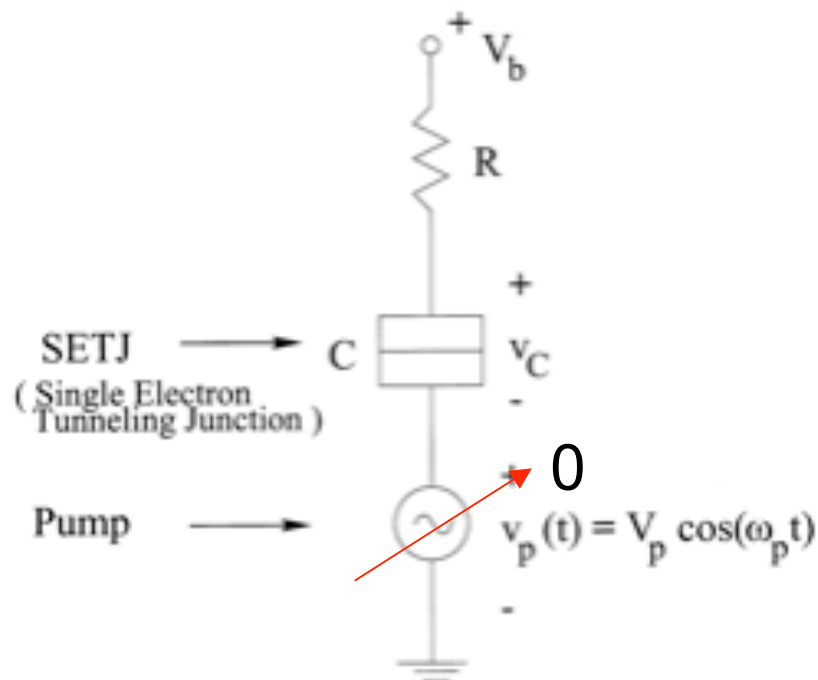


Fig. 1. An isolated driven single-electron tunneling junction circuit.

To get a feeling for the behavior of an isolated SETJ, let's first turn off the pump voltage. The behavior then resembles a relaxation oscillator.

Now, back to the isolated SETJ circuit...

To get a feeling for the behavior of an isolated SETJ, let's first turn off the pump voltage. The behavior then resembles a relaxation oscillator.

1092 T. Yang & L. O. Chua


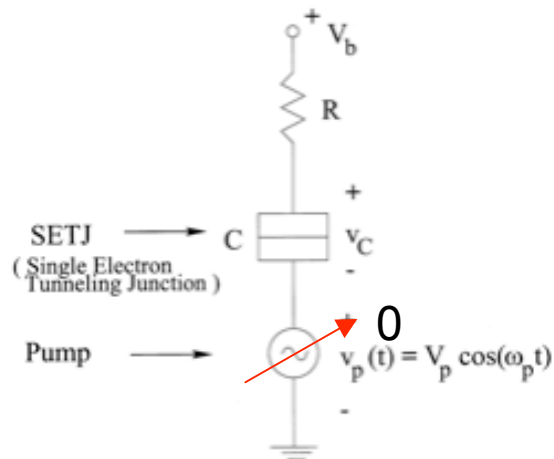


Fig. 1. An isolated driven single-electron tunneling junction circuit.

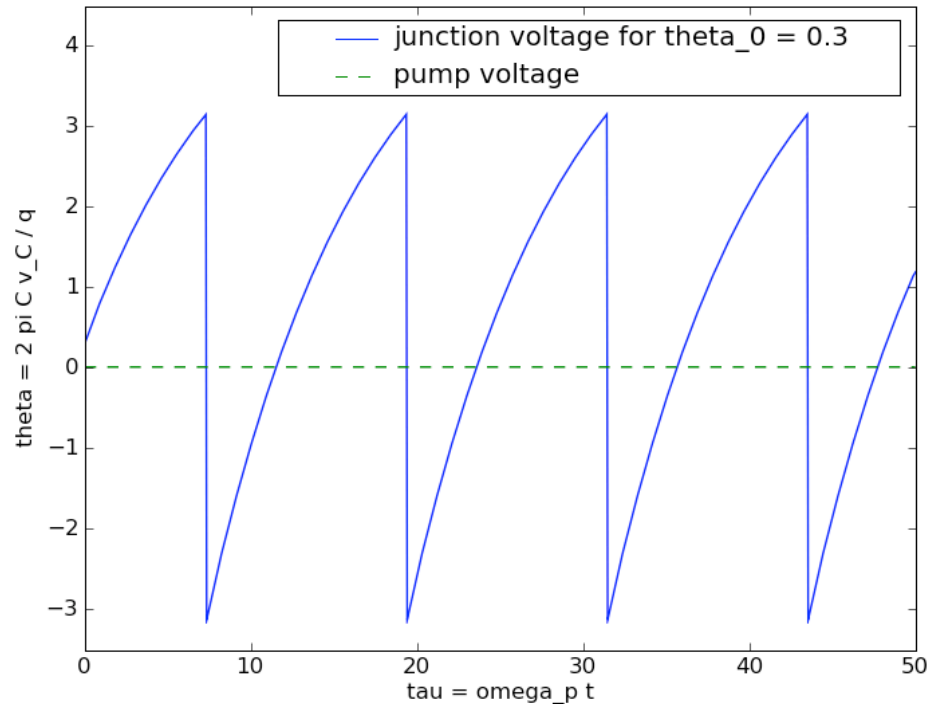isolated SETJ voltages, using fourth-order Runge-Kutta integration and impulsiv
 $a = 1.77, b = 0, \gamma = 0.333333$



Isn't it relaxing?

Now, back to the isolated SETJ circuit...

To get a feeling for the behavior of an isolated SETJ, let's first turn off the pump voltage. The behavior then resembles a relaxation oscillator.

1092 T. Yang & L. O. Chua


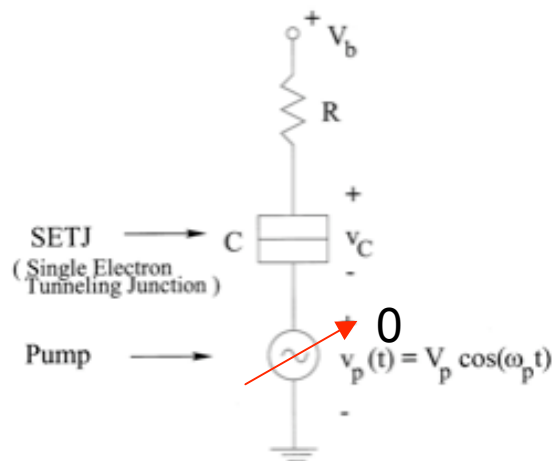


Fig. 1. An isolated driven single-electron tunneling junction circuit.

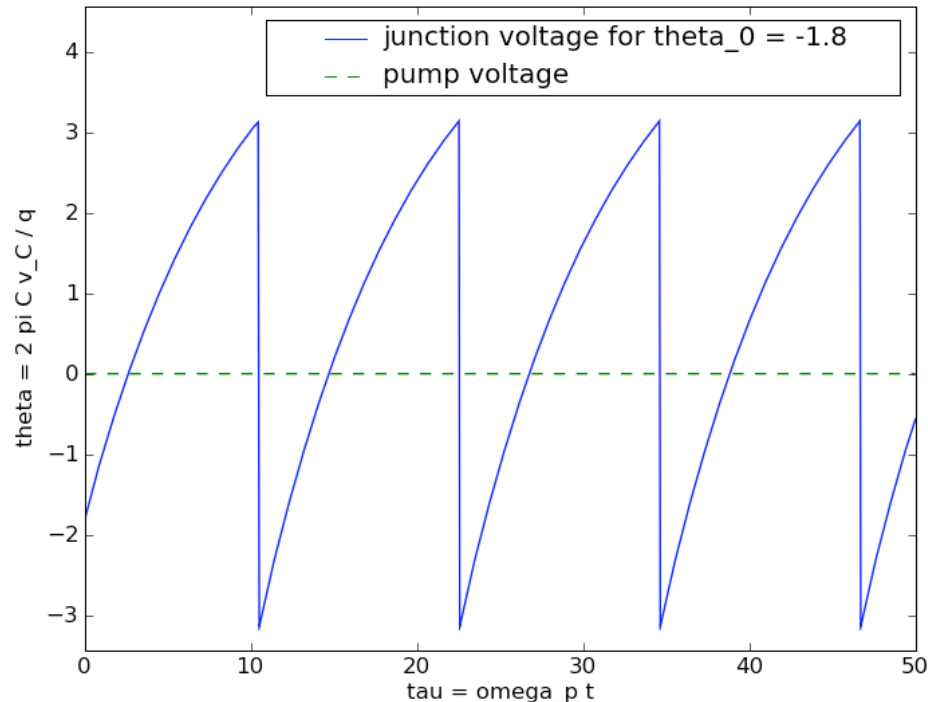isolated SETJ voltages, using fourth-order Runge-Kutta integration and impulsiv
 $a = 1.77, b = 0, \gamma = 0.333333$



Notice that there is no transient behavior for this simple setup. Also, note that changing θ_0 yields the same waveform, only shifted in time.

The isolated SETJ circuit...

1092 T. Yang & L. O. Chua


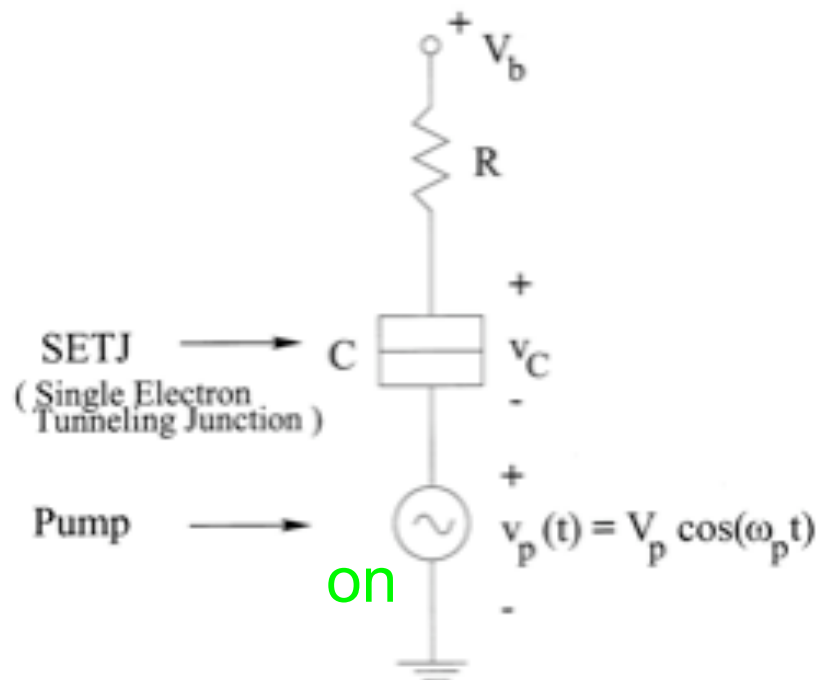


Fig. 1. An isolated driven single-electron tunneling junction circuit.

So, what happens when we turn the pump on (with a sinusoidal waveform)?


The isolated SETJ circuit...

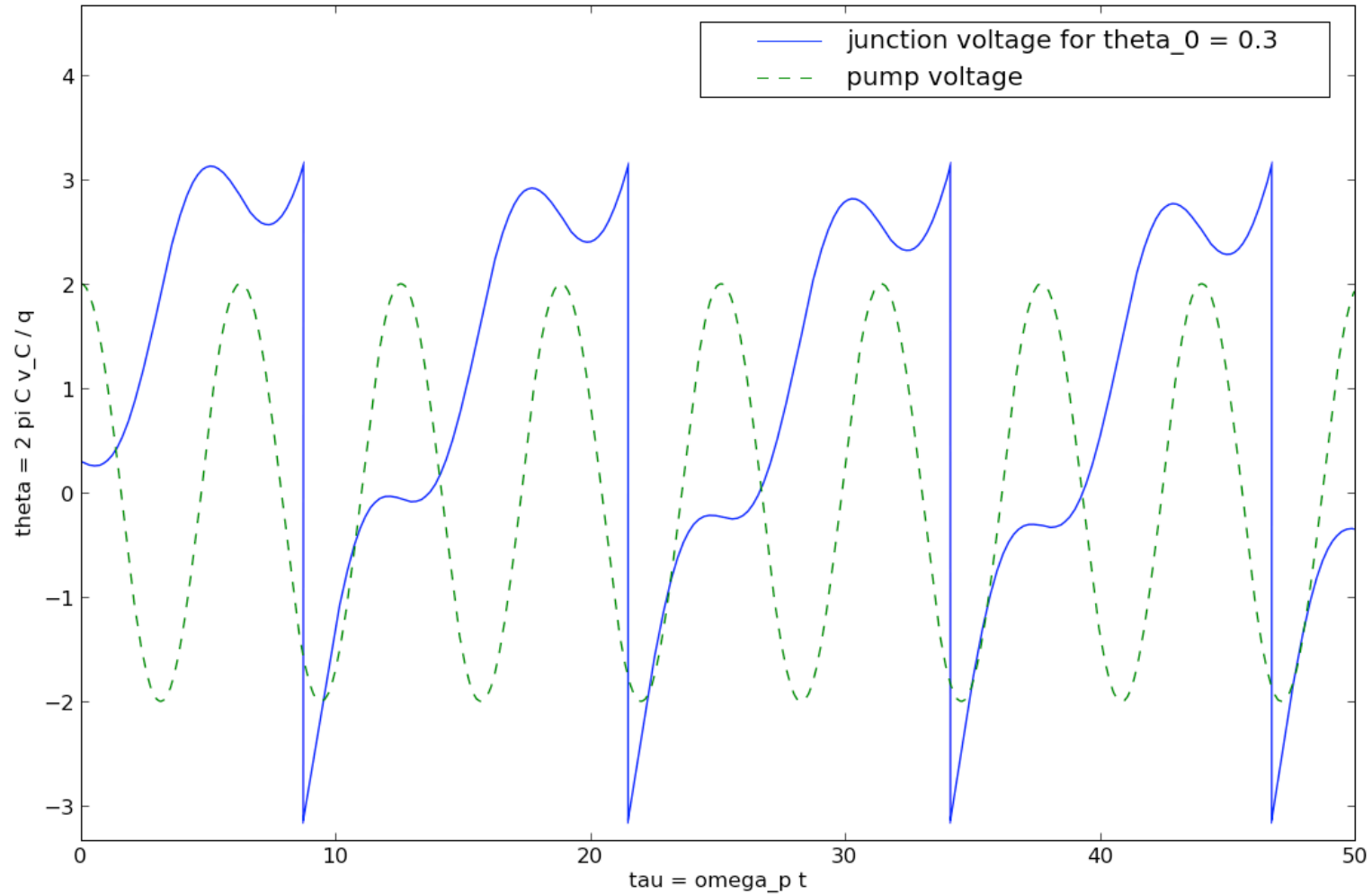time series for isolated SETJ voltages, using fourth-order Runge-Kutta integration and impulsive difference eqns
 $a = 1.77$, $b = 2$, $\gamma = 0.333333$



The isolated SETJ circuit...

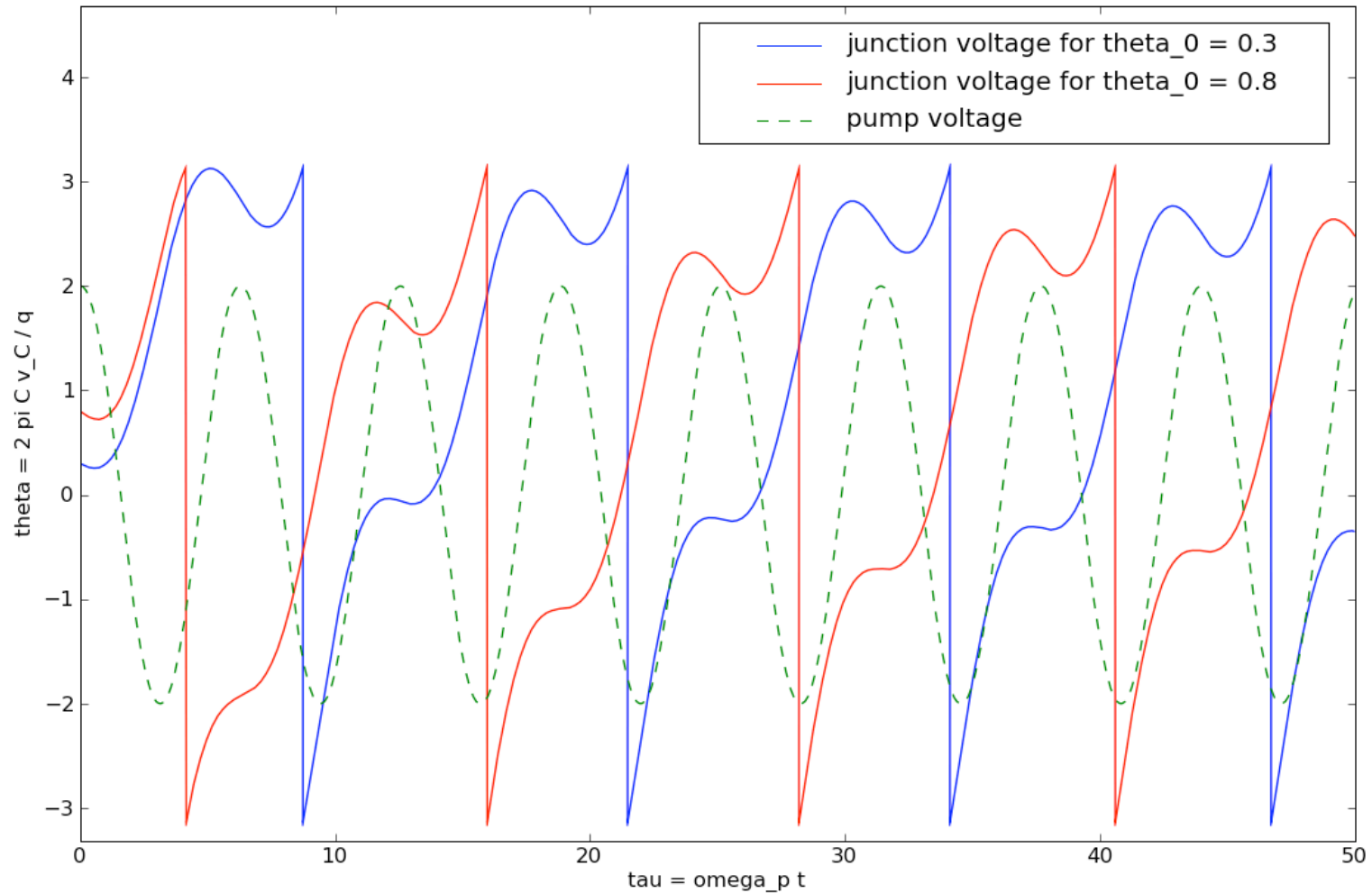time series for isolated SETJ voltages, using fourth-order Runge-Kutta integration and impulsive difference eqns
 $a = 1.77, b = 2, \text{gamma} = 0.333333$



The isolated SETJ circuit...

So, what happens when we turn the pump on (with a sinusoidal waveform)?

1092 T. Yang & L. O. Chua


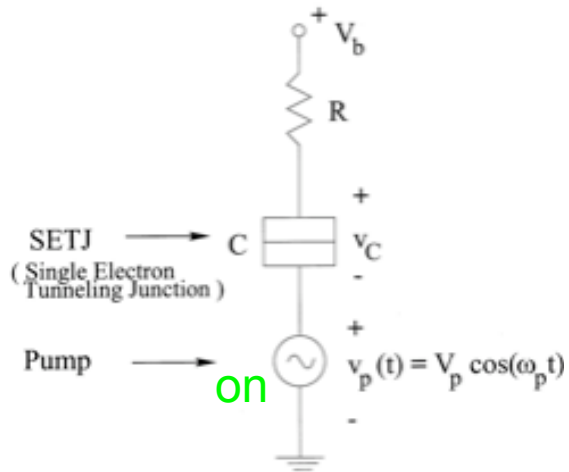


Fig. 1. An isolated driven single-electron tunneling junction circuit.

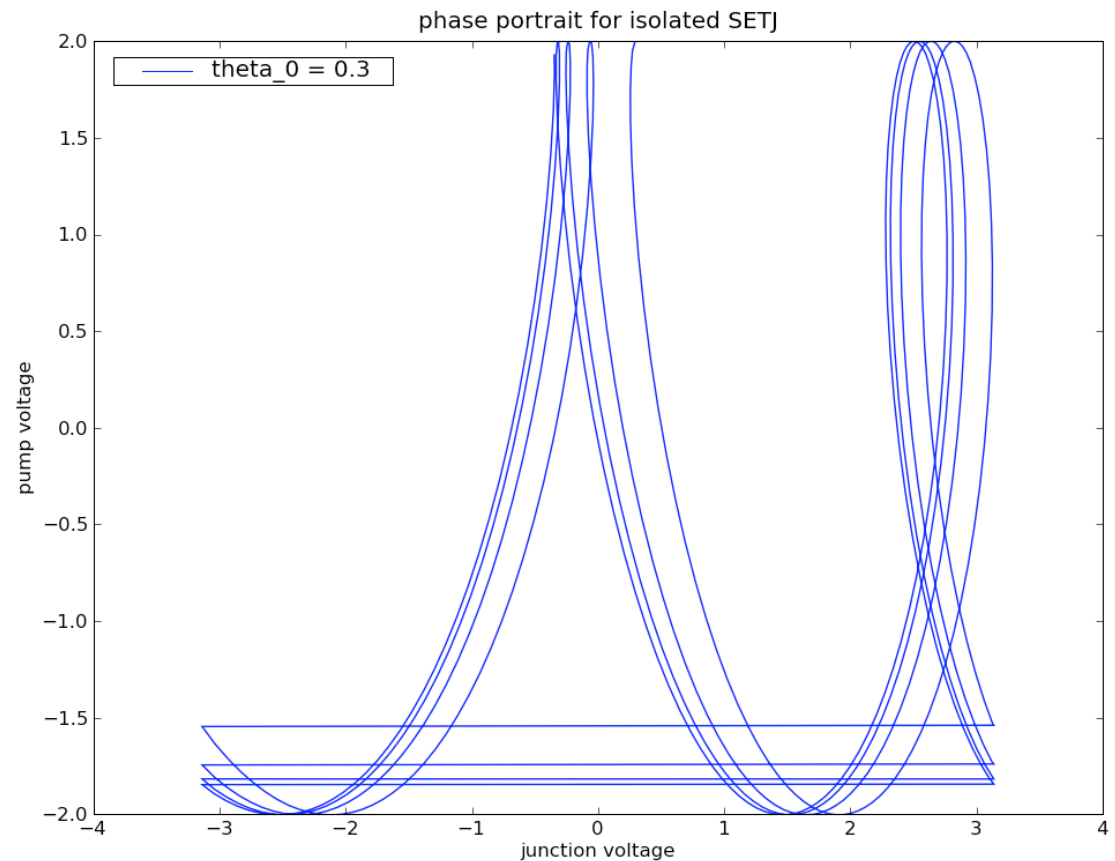

The isolated SETJ circuit...

So, what happens when we turn the pump on (with a sinusoidal waveform)?

1092 T. Yang & L. O. Chua


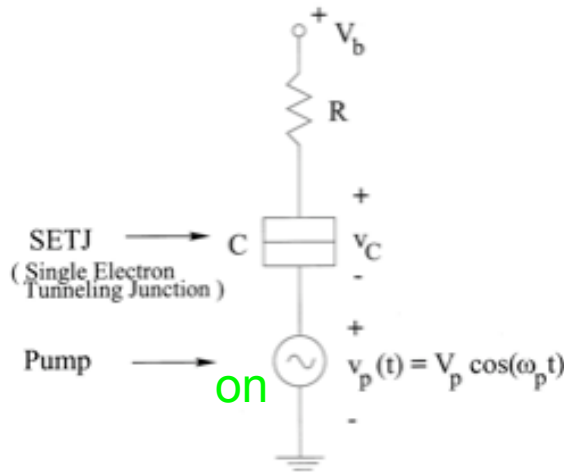


Fig. 1. An isolated driven single-electron tunneling junction circuit.

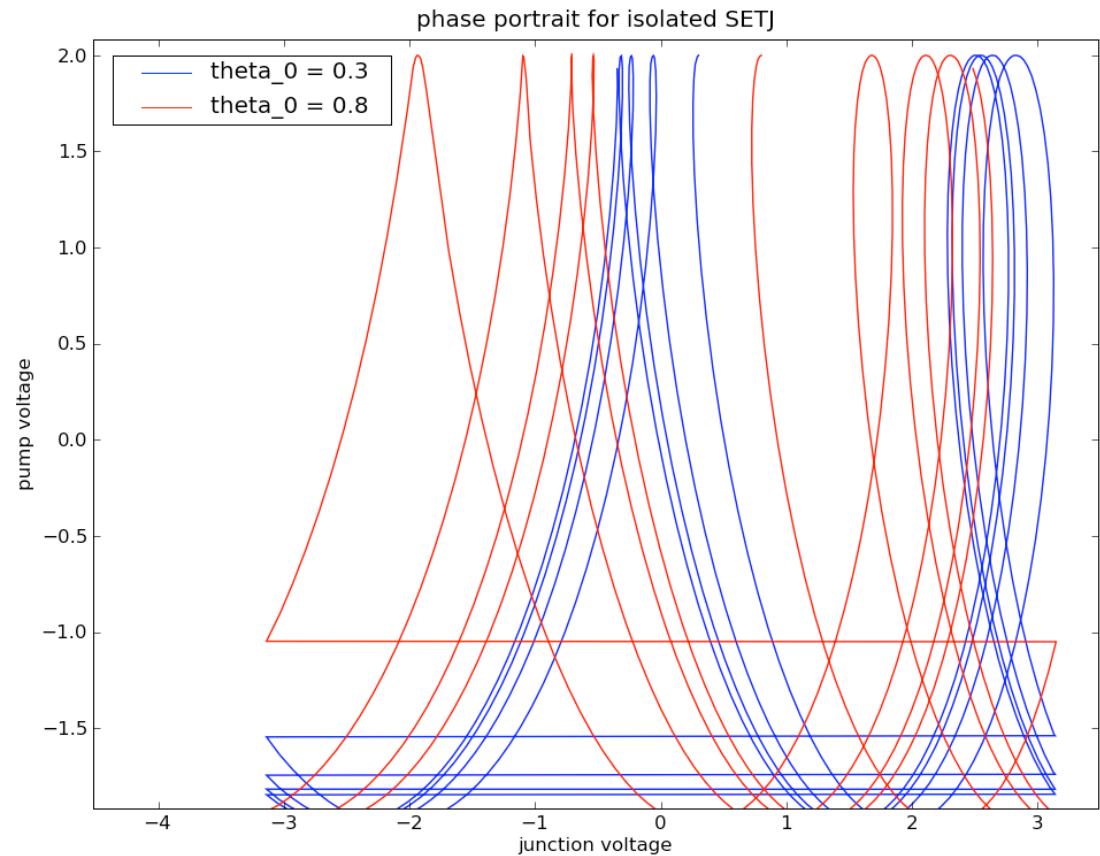

The isolated SETJ circuit...

So, what happens when we turn the pump on (with a sinusoidal waveform)?

1092 T. Yang & L. O. Chua



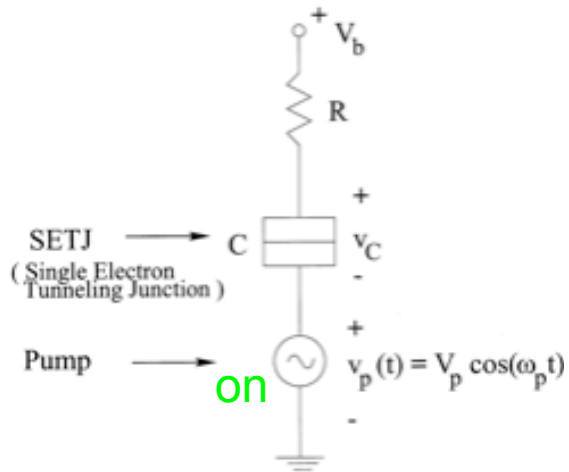


Fig. 1. An isolated driven single-electron tunneling junction circuit.

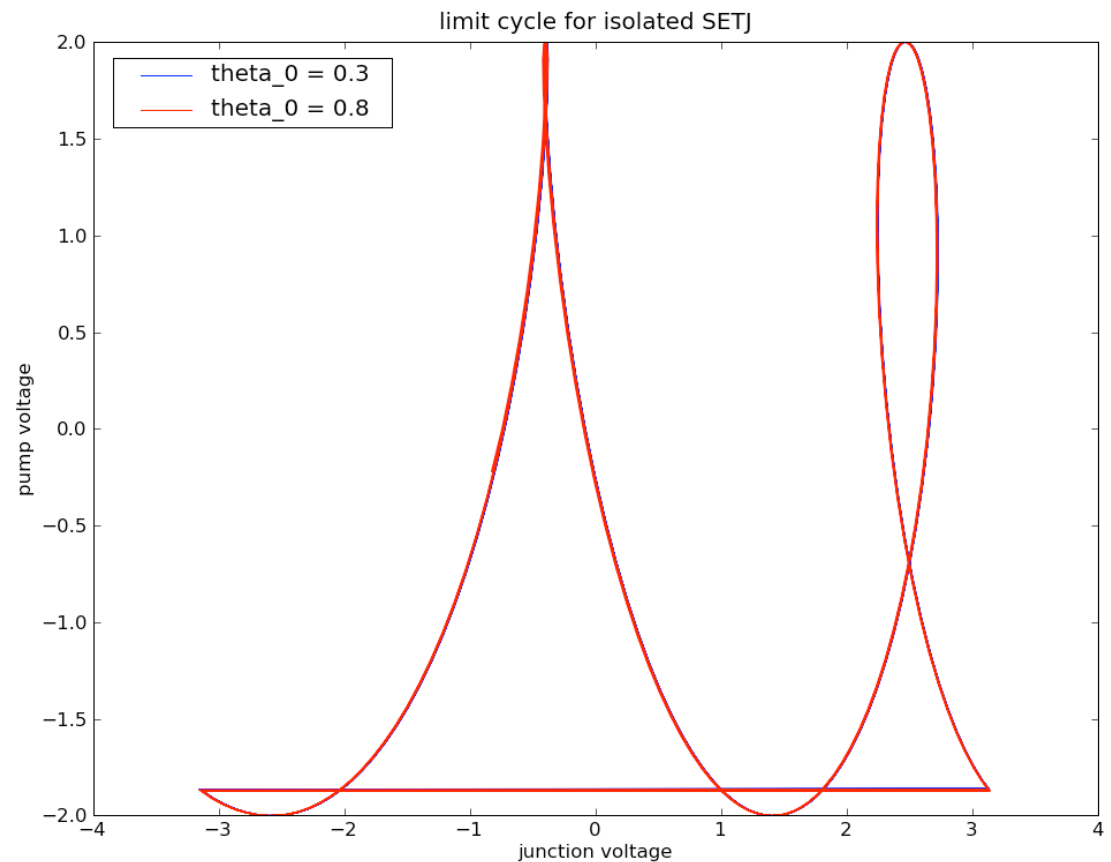


The isolated SETJ circuit...

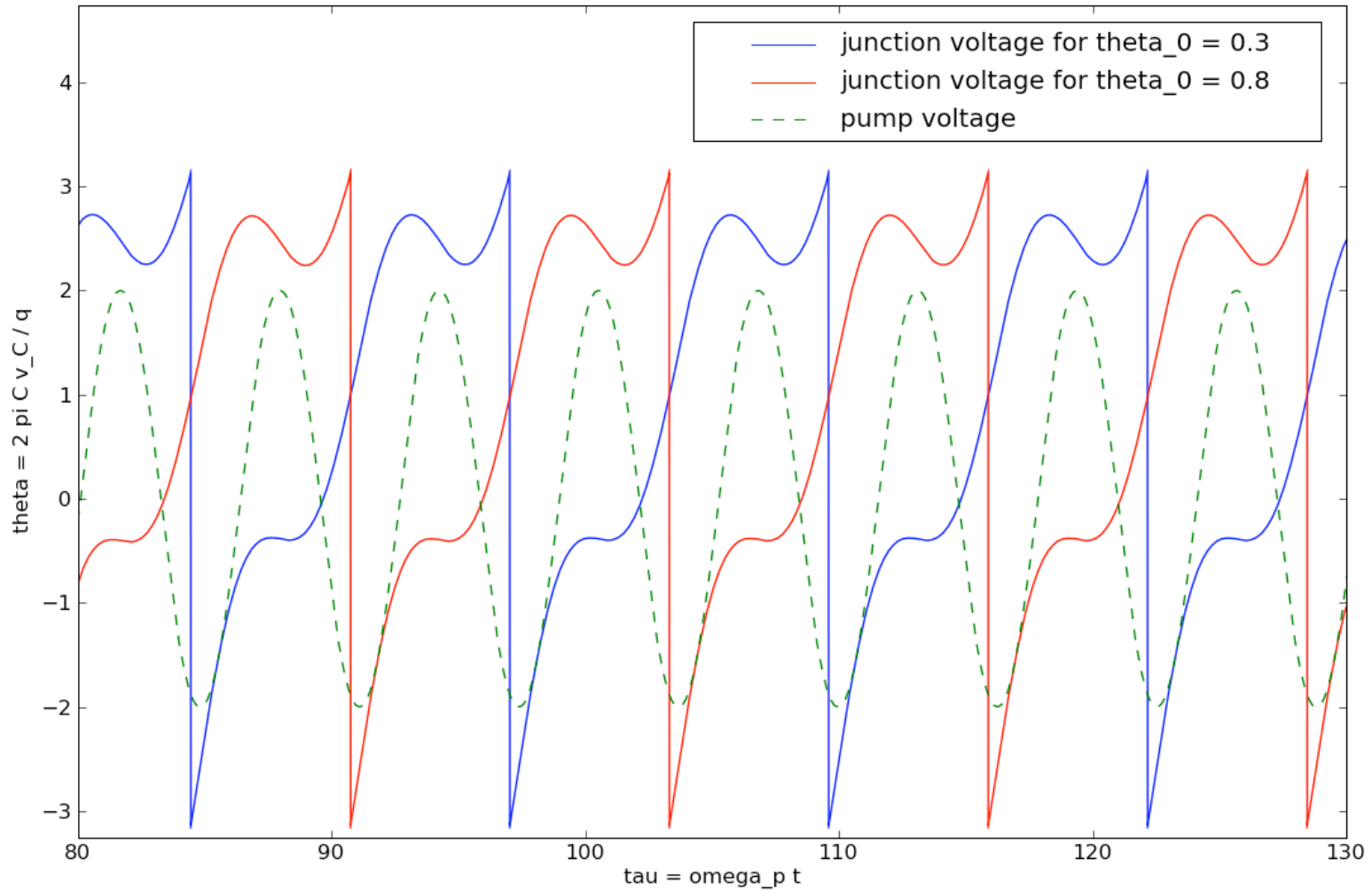time series for isolated SETJ voltages, using fourth-order Runge-Kutta integration and impulsive difference eqns
 $a = 1.77, b = 2, \text{gamma} = 0.333333$



The isolated SETJ circuit...

1092 T. Yang & L. O. Chua

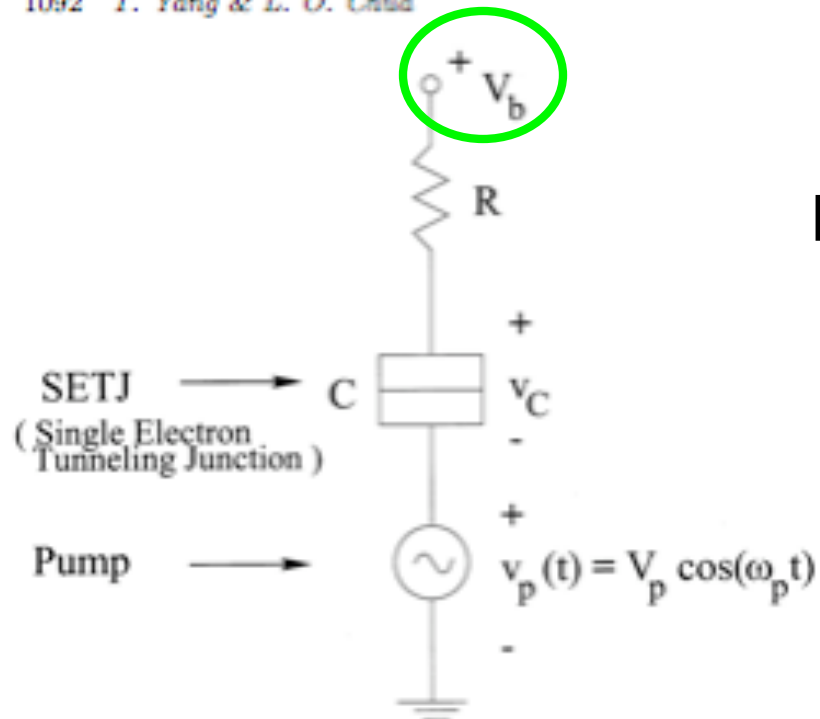

Next parameter to mess with:


$$\alpha = V_b / V_t$$

Fig. 1. An isolated driven single-electron tunneling junction circuit.

$$(V_t = e / 2C)$$


The isolated SETJ circuit...

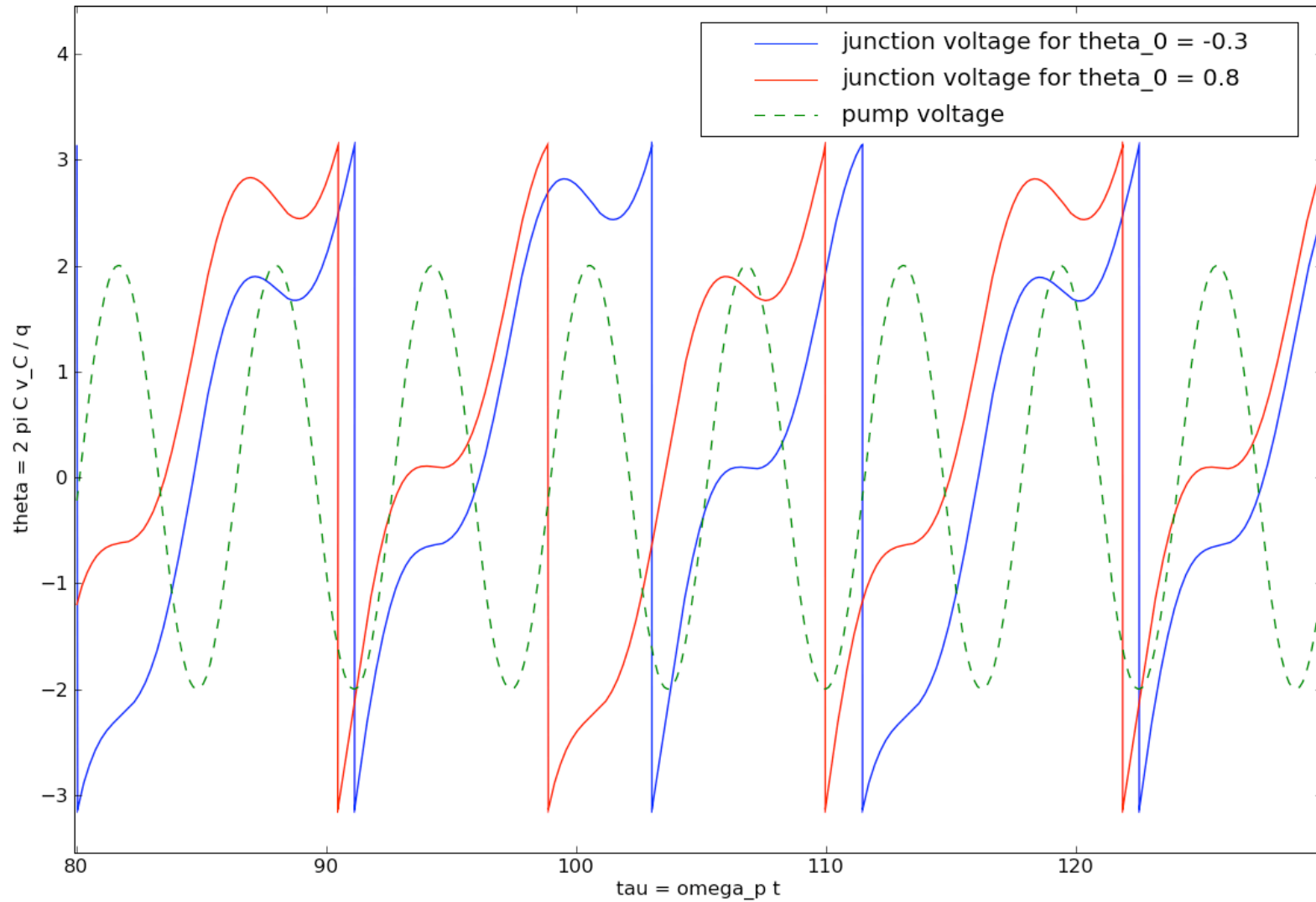time series for isolated SETJ voltages, using fourth-order Runge-Kutta integration and impulsive difference eqns
 $a = 1.95$, $b = 2$, $\gamma = 0.333333$




The isolated SETJ circuit...

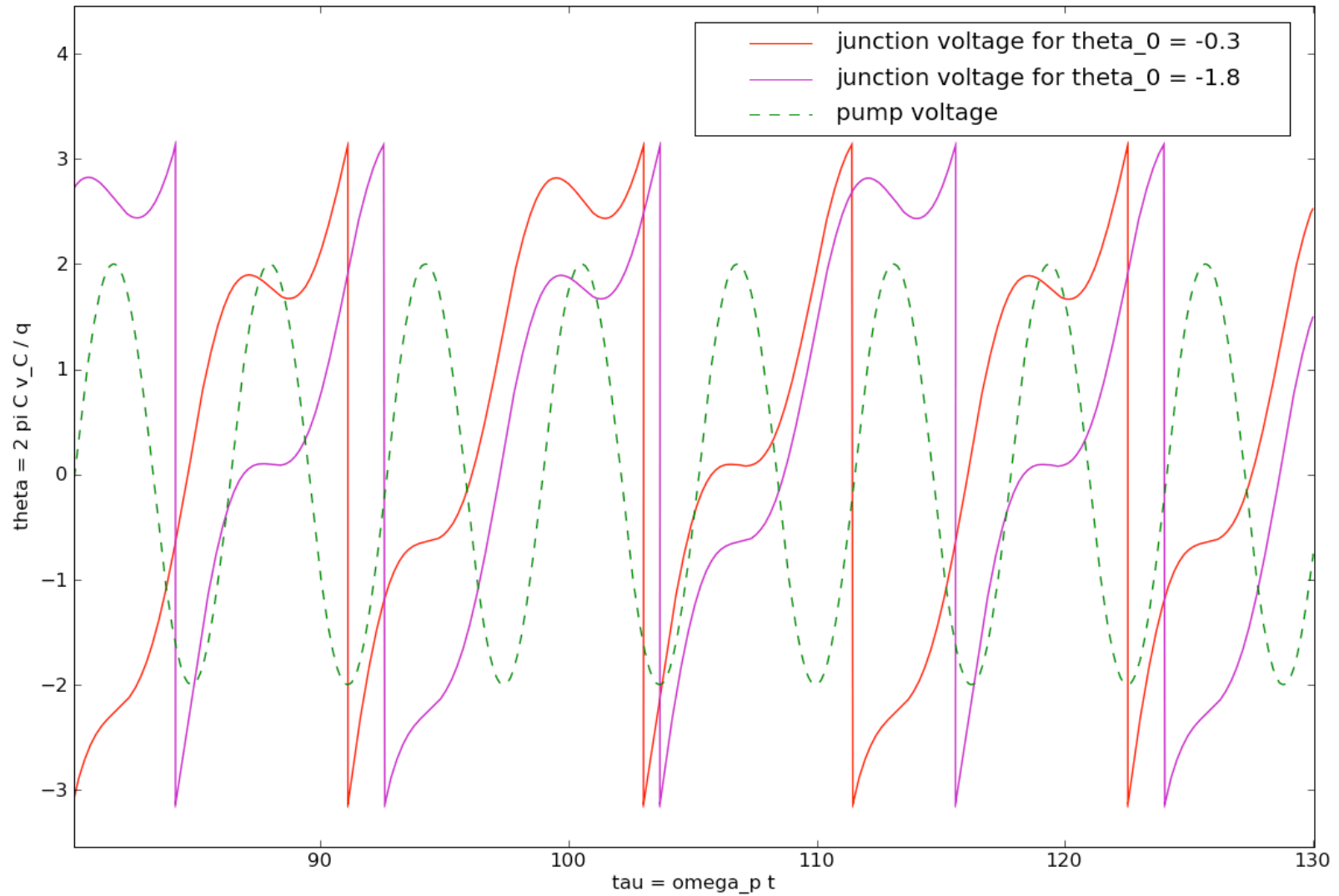time series for isolated SETJ voltages, using fourth-order Runge-Kutta integration and impulsive difference eqns
a = 1.95, b = 2, gamma = 0.333333




The isolated SETJ circuit...

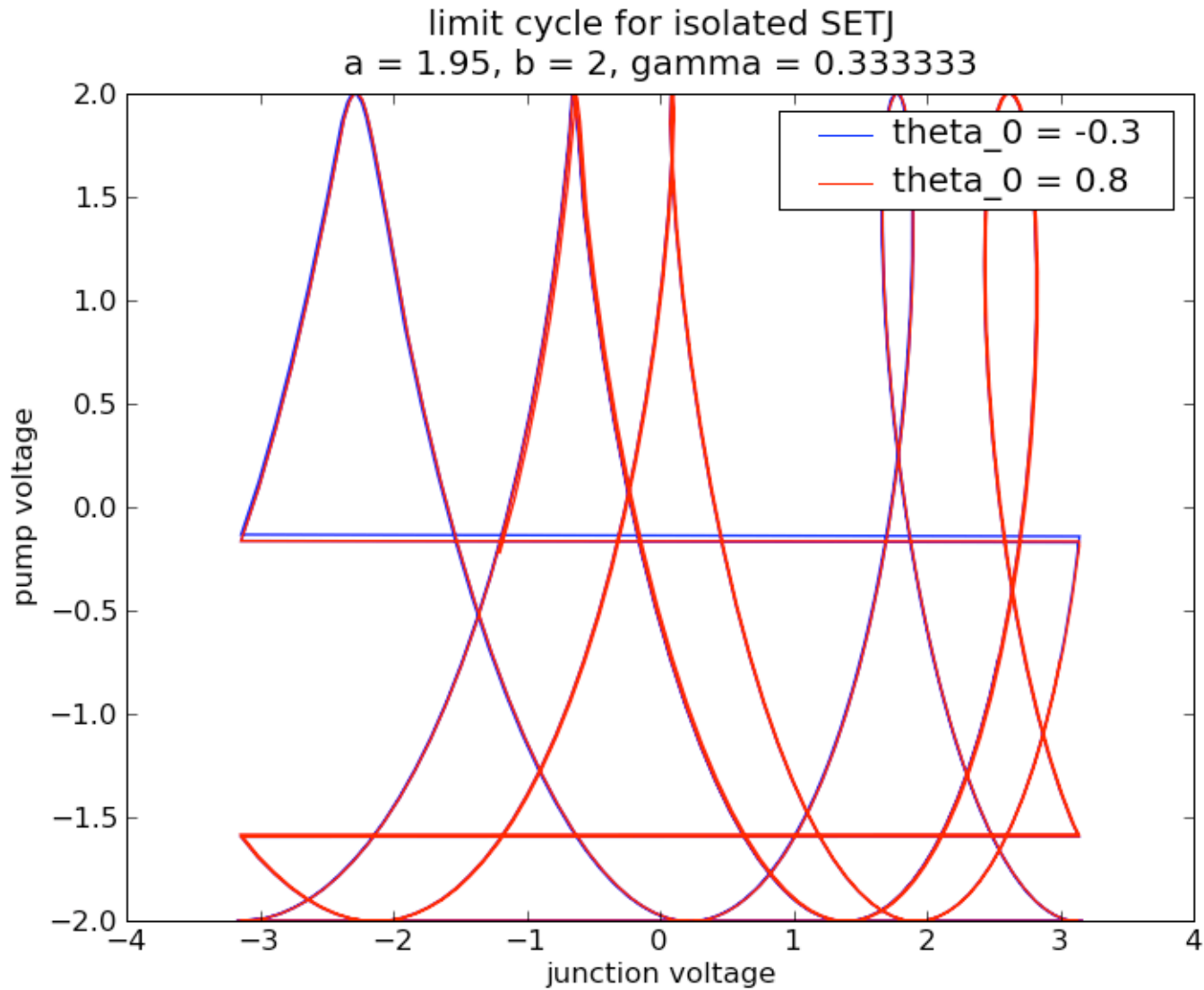


The isolated SETJ circuit..

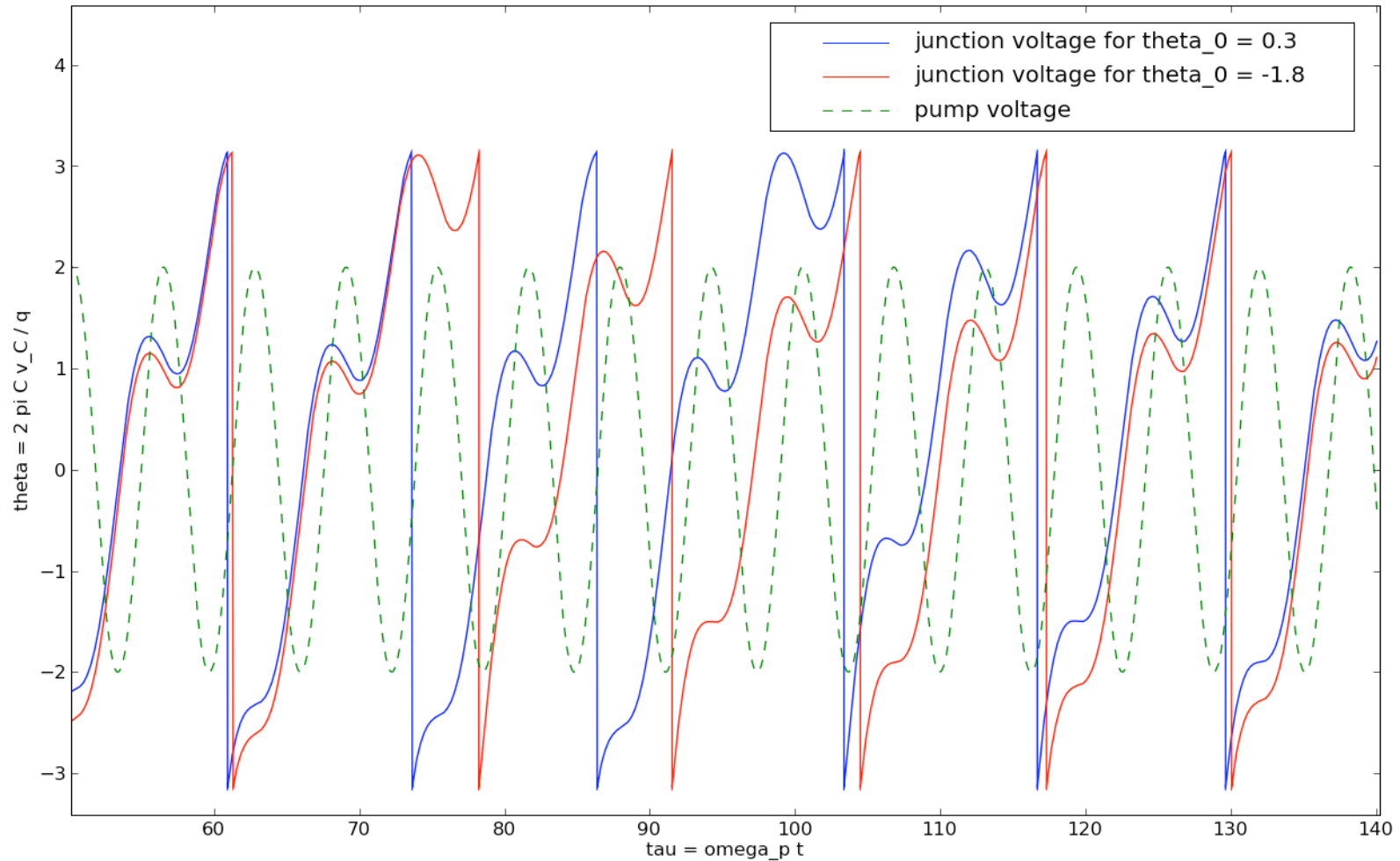
time series for isolated SETJ voltages, using fourth-order Runge-Kutta integration and impulsive difference eqns
 $a = 1.49$, $b = 2$, $\gamma = 0.333333$




The isolated SETJ circuit...

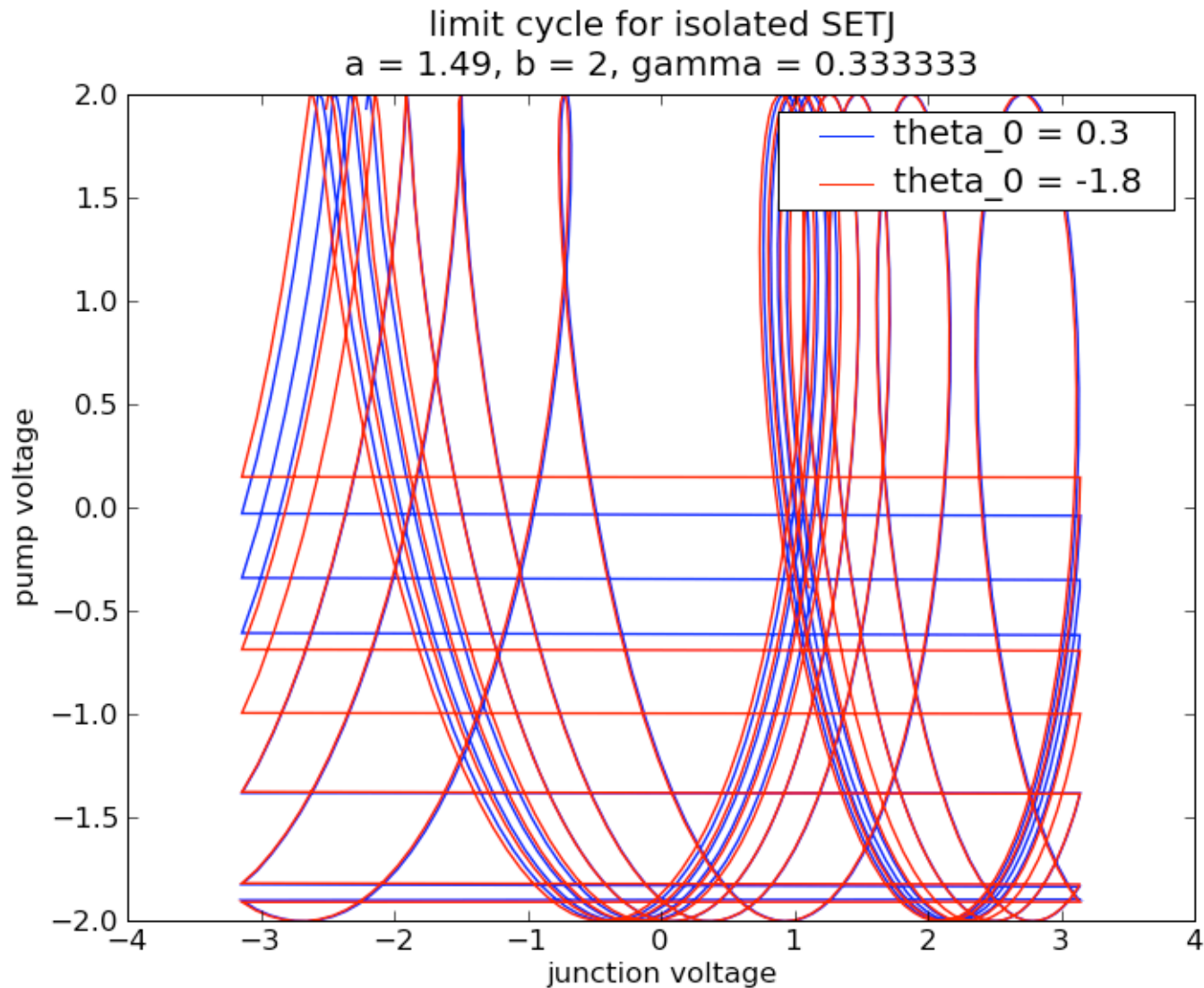

The isolated SETJ circuit...

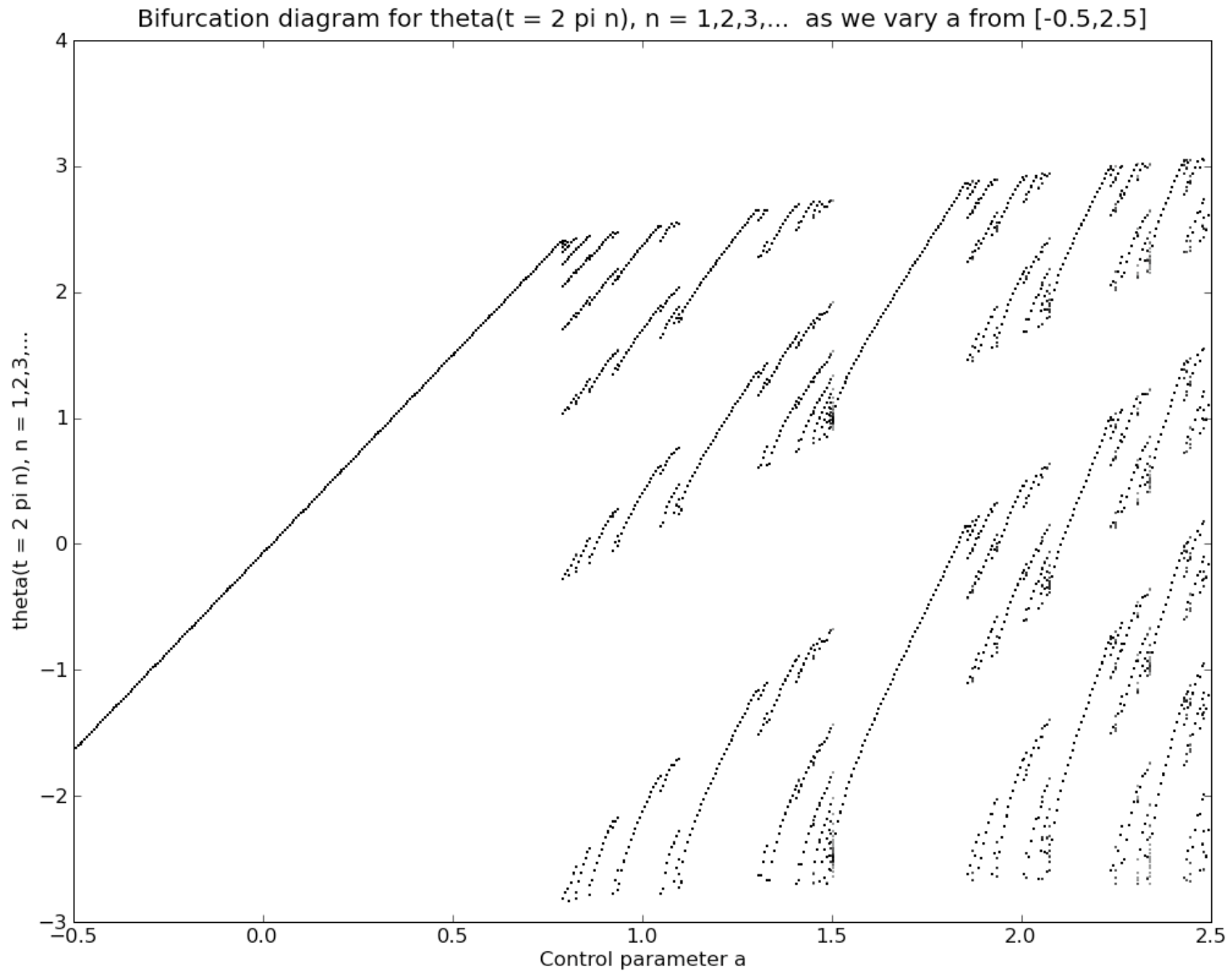


And now, for a two-coupled SETJ circuit

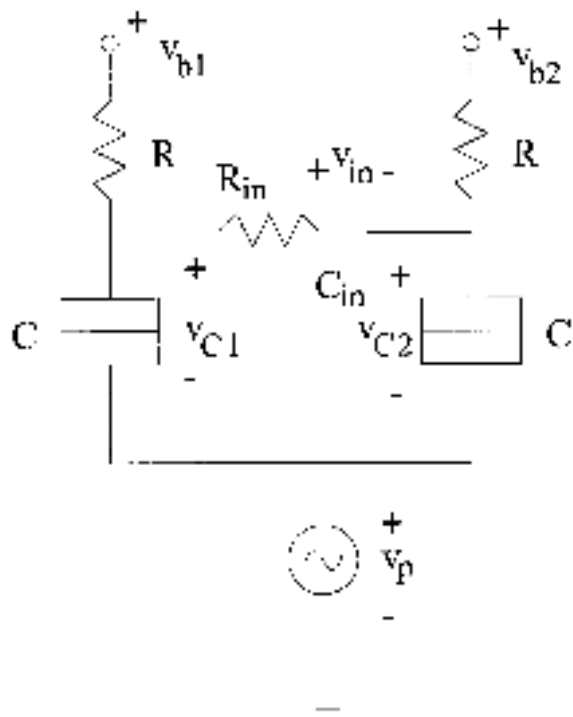


And now, for a two-coupled SETJ circuit

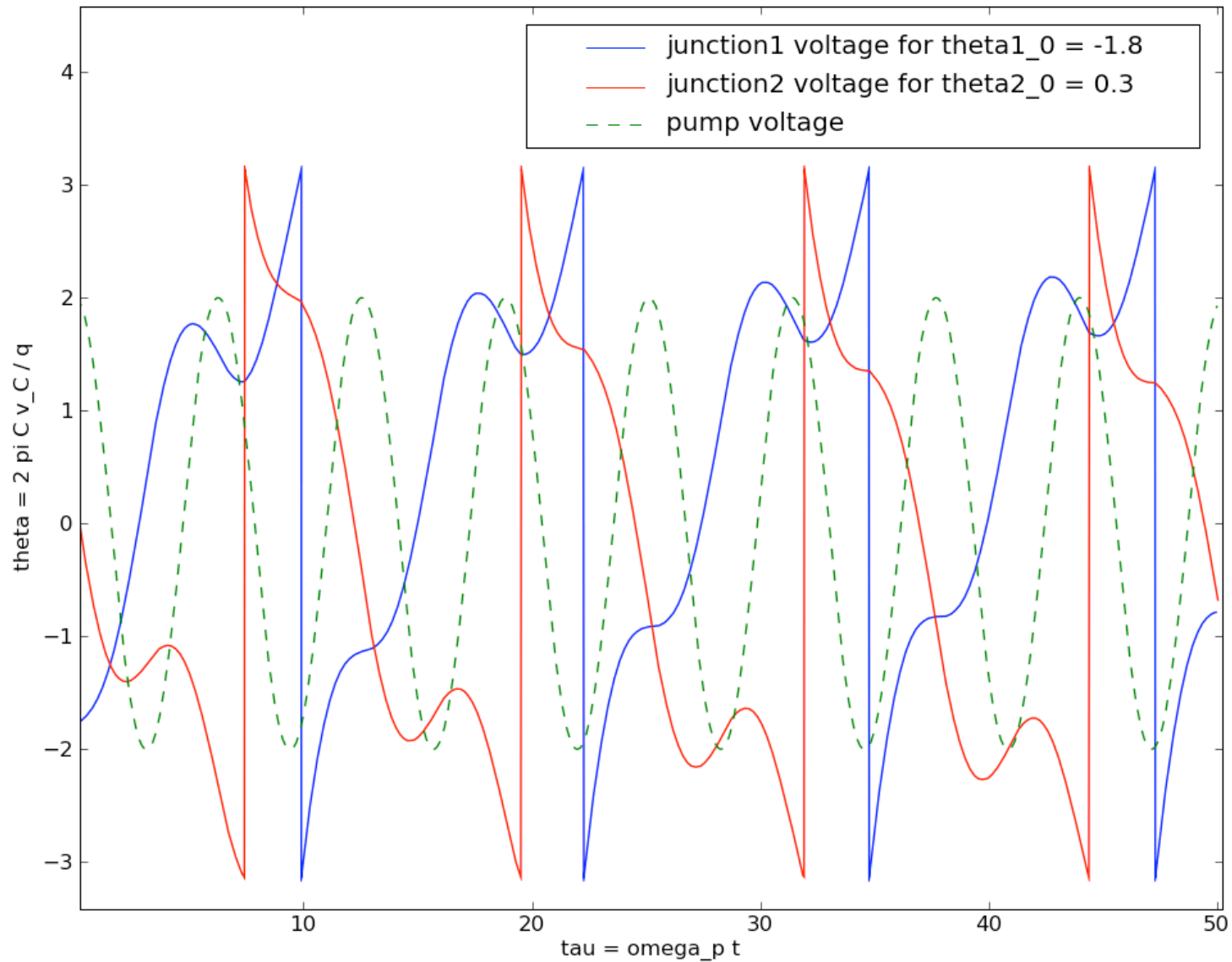time series for two-coupled SETJ voltages, using fourth-order Runge-Kutta integration and impulsive difference eq
 $a = [1.77, -1.77]$, $b = 2$, $\gamma = 0.333333$



And now, for a two-coupled SETJ circuit

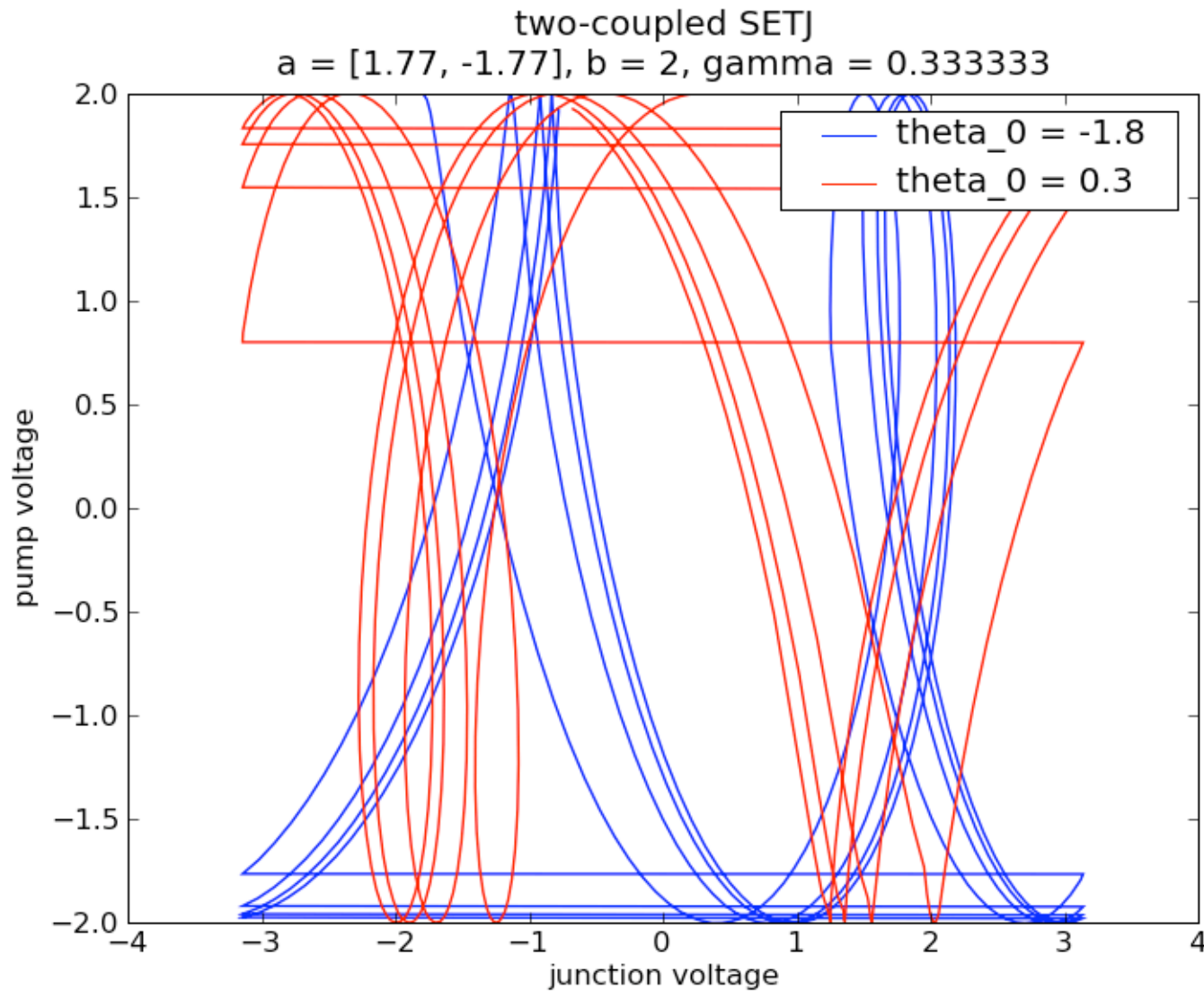

And now, for a two-coupled SETJ circuit

