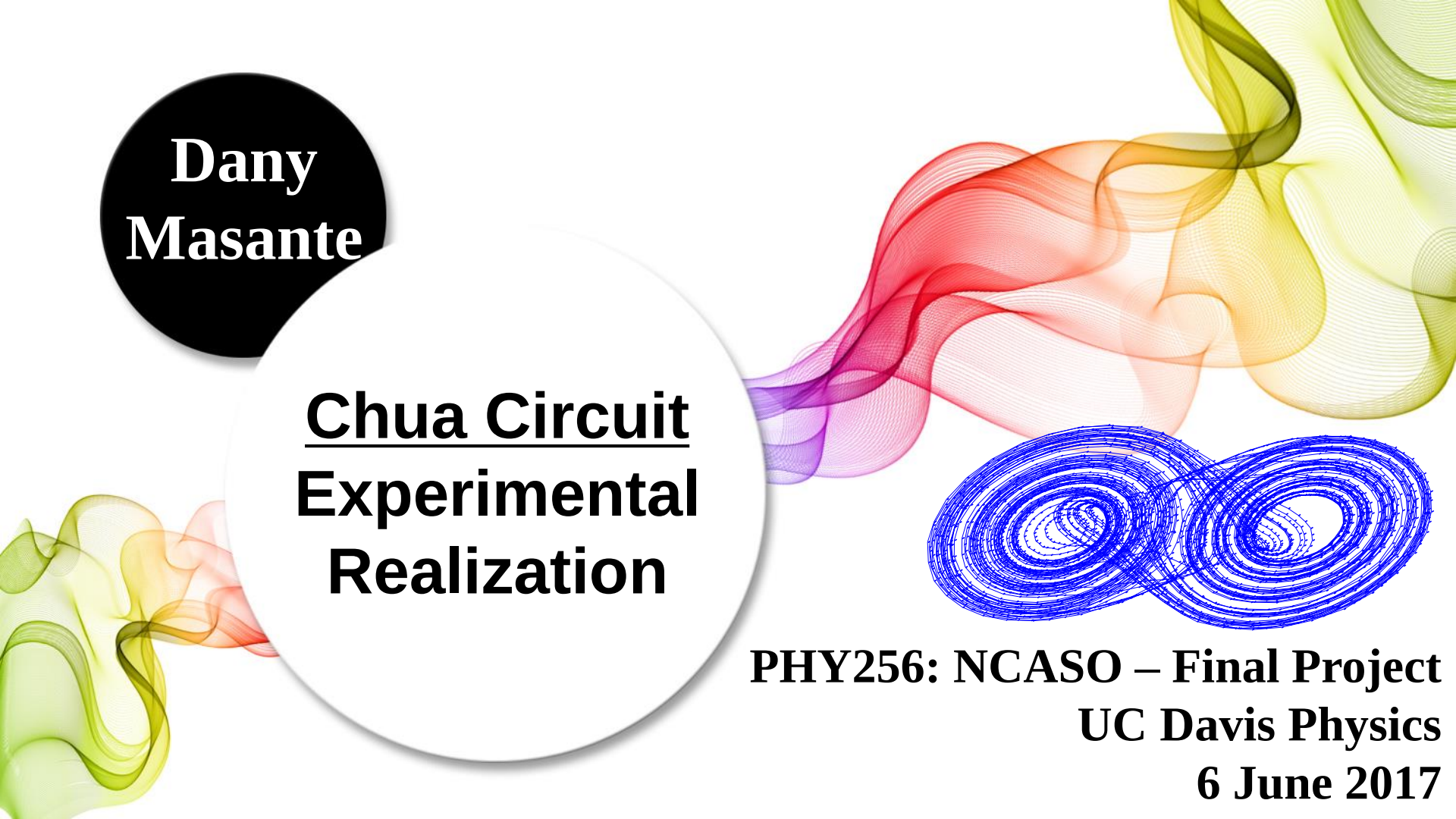





**Dany
Masante**

**Chua Circuit
Experimental
Realization**


**PHY256: NCASO – Final Project
UC Davis Physics
6 June 2017**

1

Chua's Circuit

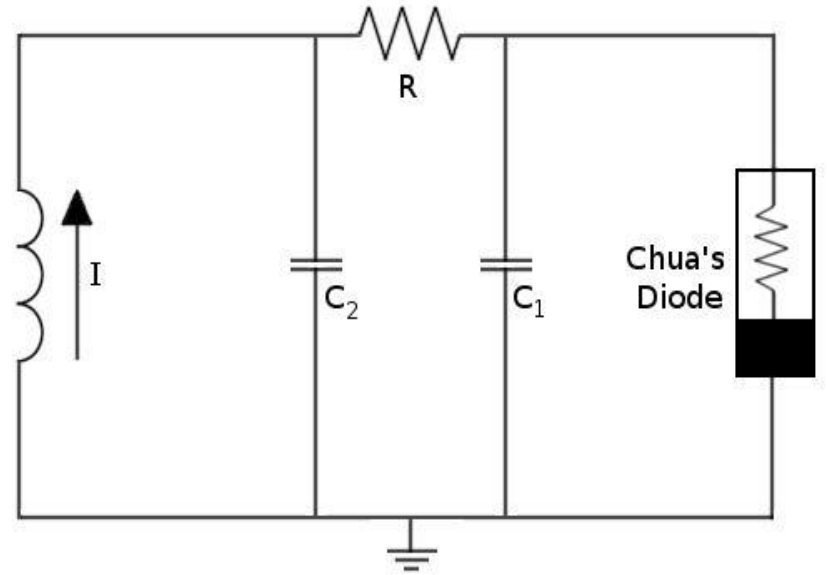


The equations of motion

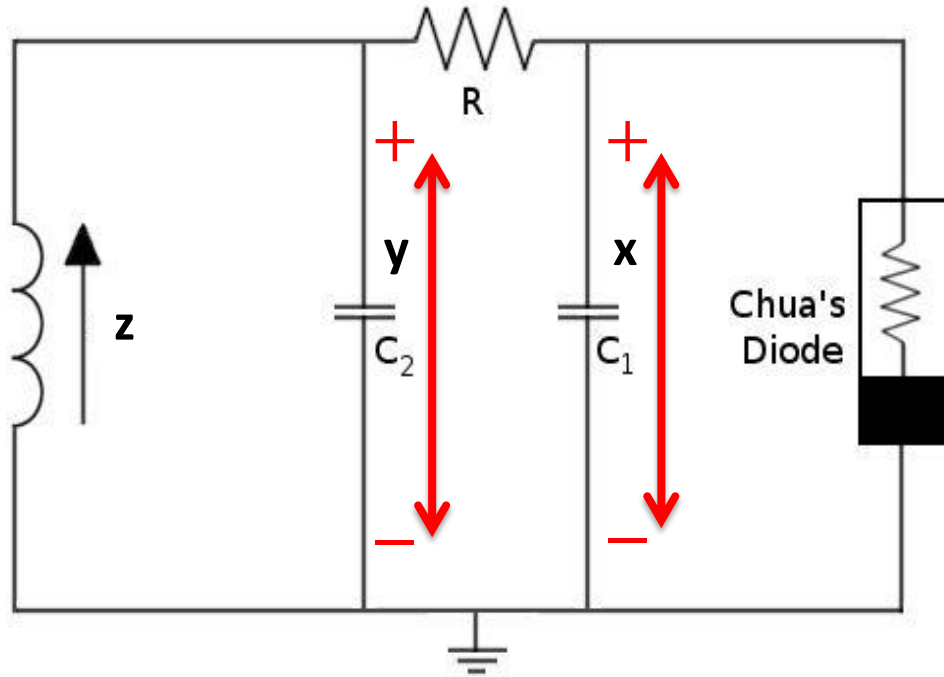

$$\dot{x}'' \rightarrow \frac{dV_1}{dt} = \left[\frac{1}{RC_1} \right] ((V_2 - V_1) - R * g(v_1))$$


$$\dot{y}'' \rightarrow \frac{dV_2}{dt} = \left[\frac{1}{RC_2} \right] ((V_1 - V_2) - R * i_L)$$
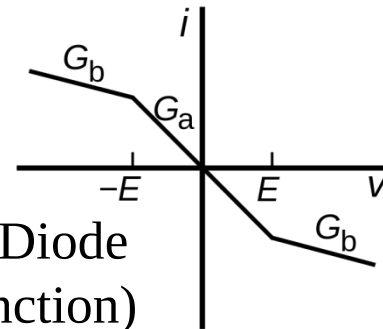
$$\dot{z}'' \rightarrow \frac{di_L}{dt} = \left[\frac{1}{L} \right] (-v_2)$$




Where $g(x)$ is Chua's Diode
(piecewise function)


Three Fixed Points

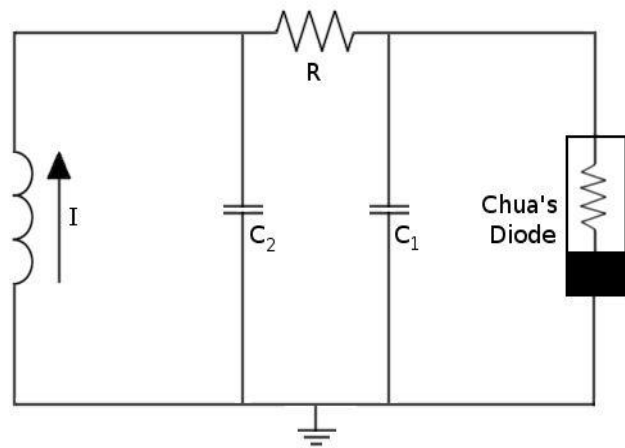

$$p_0 = [0, \quad 0, \quad 0]$$

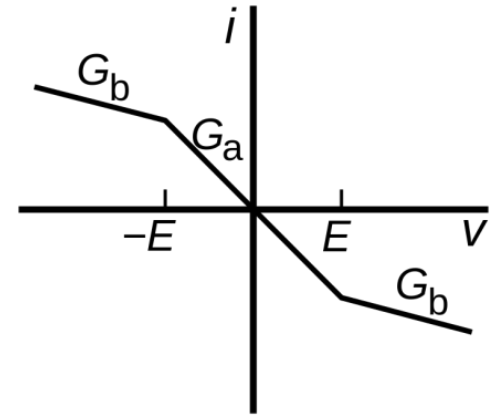


$$p_{1,2} = \pm \left[\frac{-E(G_b - G_a)(r_L + R)}{1 + (R + r_L)G_b}, \quad \frac{-E(G_b - G_a)(r_L)}{1 + (R + r_L)G_b}, \quad \frac{+E(G_b - G_a)(r_L)}{1 + (R + r_L)G_b} \right]$$

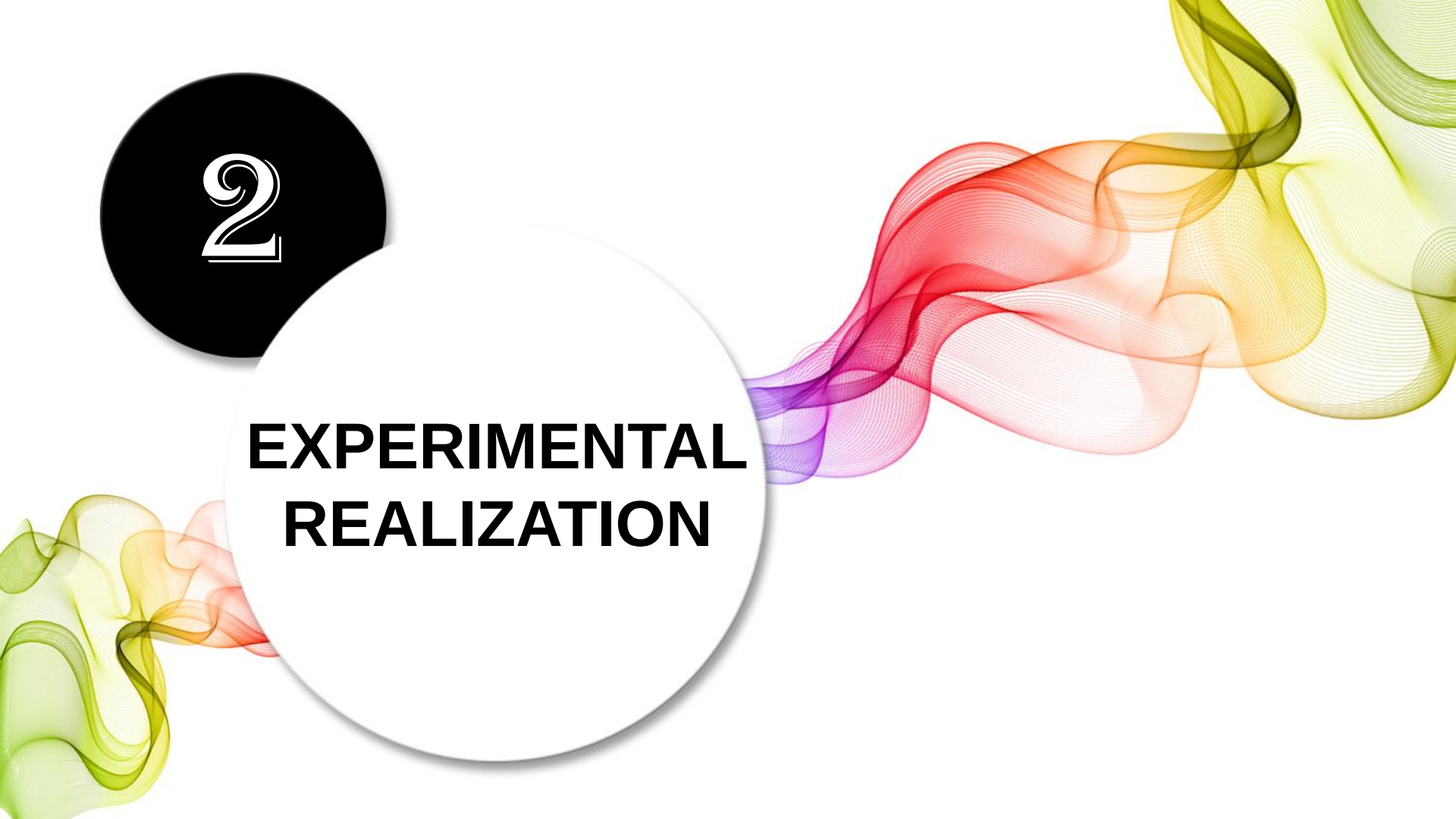The background features abstract, flowing, wavy lines in shades of green, yellow, orange, and red. A large white circle is centered on the page, containing the text 'EXPERIMENTAL REALIZATION'. In the top-left corner, there is a black circle containing the number '2'.

2

EXPERIMENTAL REALIZATION

Experimental Realization

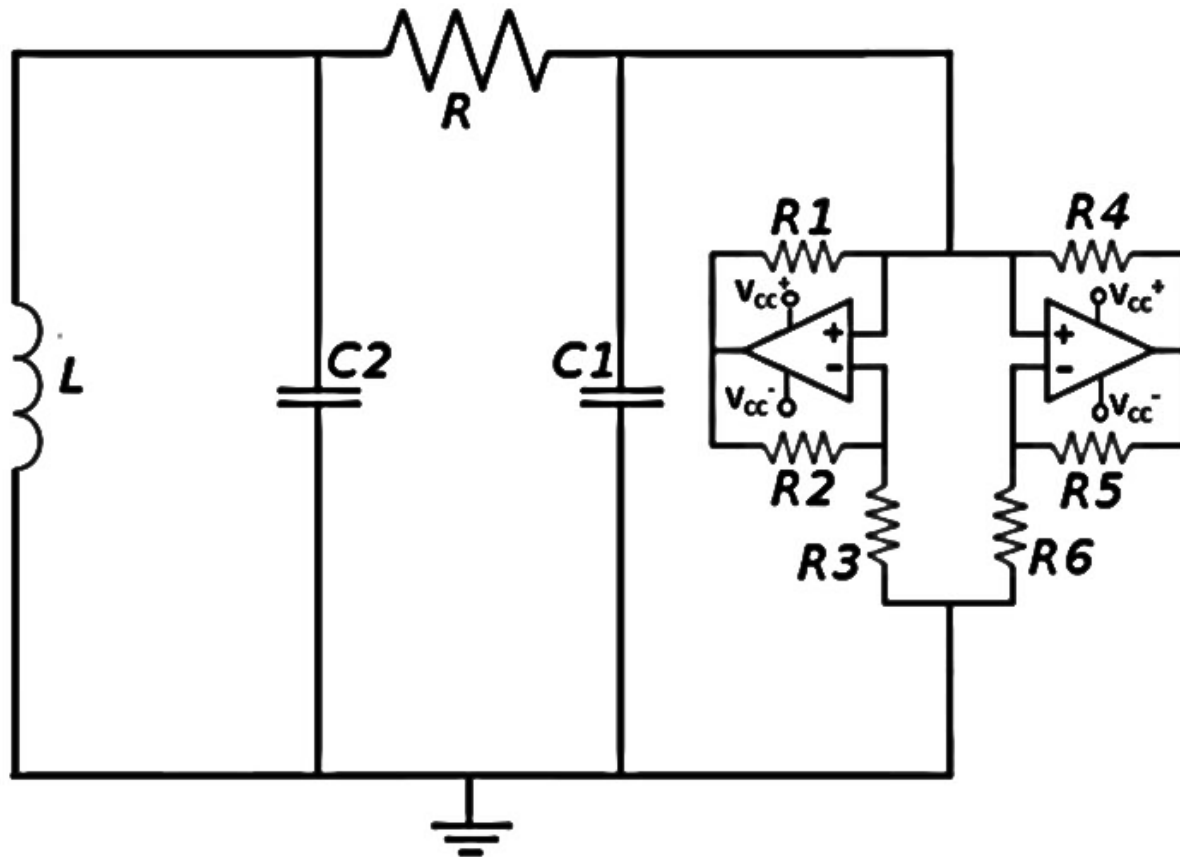

Where

$$R_1 = 220 \text{ } [\Omega]$$

$$R_2 = 220 \text{ } [\Omega]$$

$$R_3 = 2.2 \text{ } [k\Omega]$$

$$R_4 = 22 \text{ } [k\Omega]$$

$$R_5 = 22 \text{ } [k\Omega]$$

$$R_6 = 3.3 \text{ } [k\Omega]$$

$$C_1 = 10 \text{ } [nF]$$



$$C_2 = 100 \text{ } [nF]$$

$$L = 18 \text{ } [mH]$$

And R is a potentiometer
(variable resistor)

Chua Diode
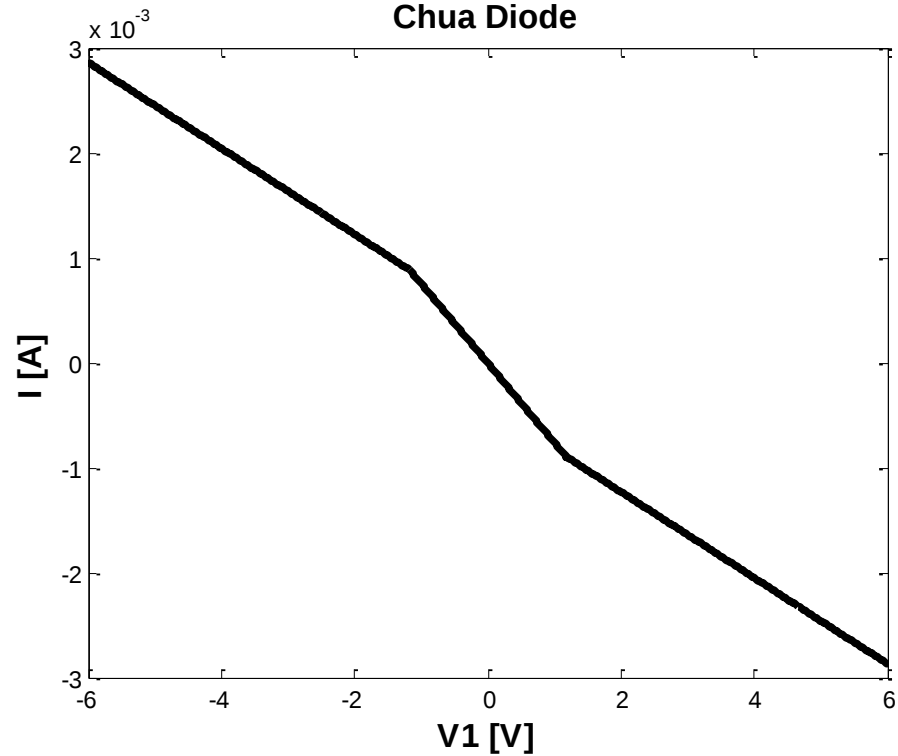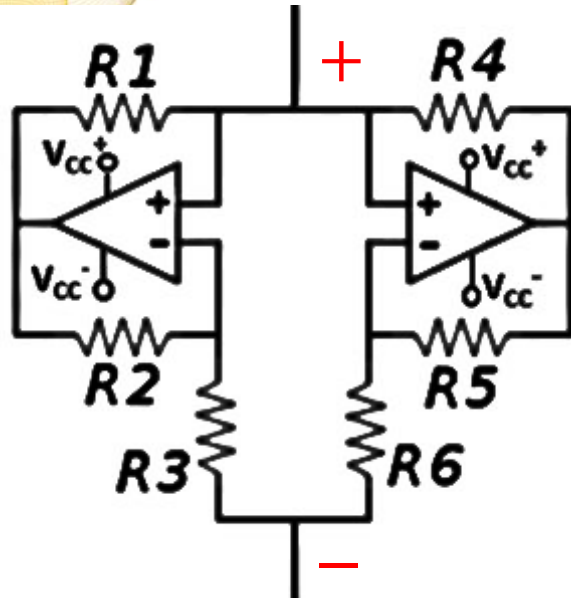
$$g(v_1) = \begin{cases} m_0 v_1 + (m_0 - m_1)E_1, & v_1 \leq -E_1 \\ m_1 v_1, & -E_1 \leq v_1 \leq E_1 \\ m_0 v_1 + (m_1 - m_0)E_1, & v_1 \geq E_1 \end{cases}$$



Where


$$m_0 = \frac{1}{R_4} - \frac{1}{R_3}, \quad m_1 = -\frac{1}{R_3} - \frac{1}{R_6}, \quad E_1 = \frac{R_3}{(R_2 + R_3)} E_{sat}$$

List of Materials

Device	Stock Code	Quantity	Description
Capacitor	Mapln Sc Series	2	Metallized Polyester Film (MKT) Capacitors
Inductor	PCH45X186KLT	1	Axial Lead Power Choke
Resistor	TOPCOFRLD008	6	Metal Film full range resistor
Potentiometer	B01LYHMKNN	1	Logarithmic Dual Rotary Potentiometer
Operational Amplifier	TI6PCSUA741CP	2	General Purpose Operational Amplifier

All elements are Rohs complilant

Experimental Realization

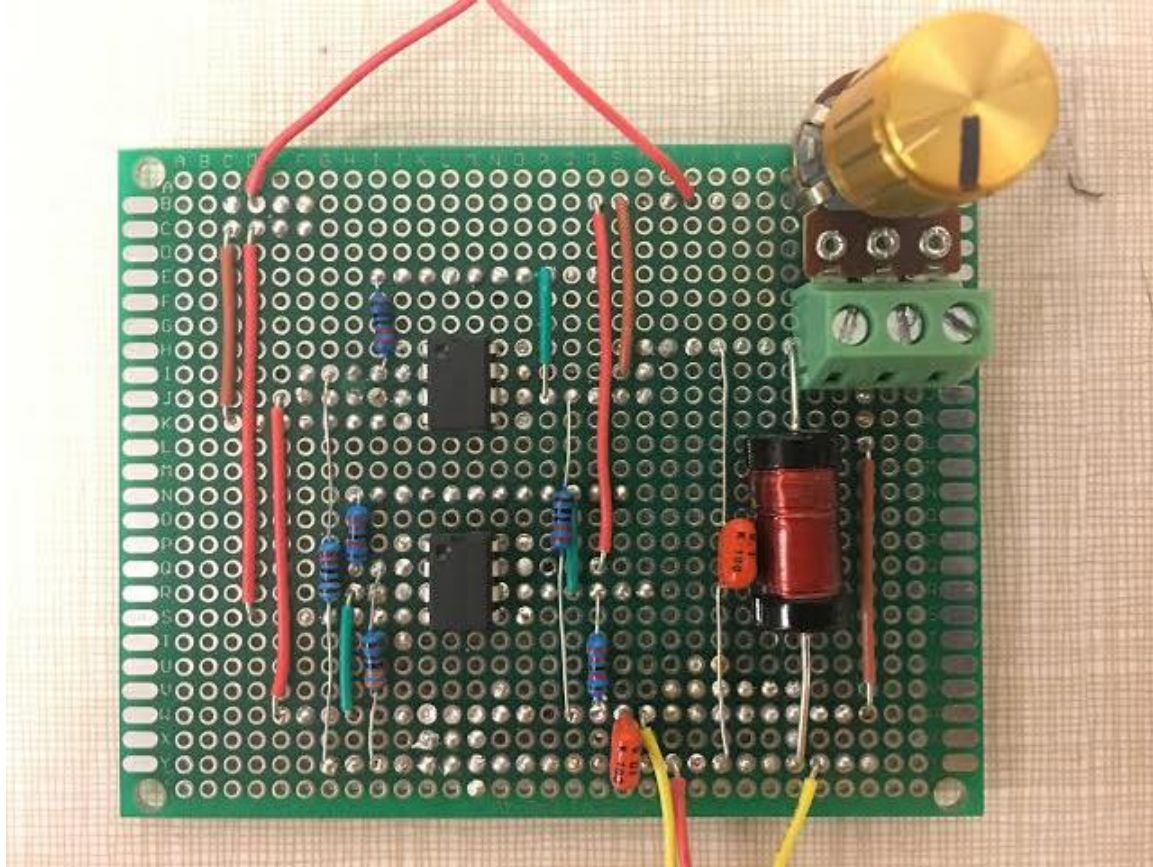

3

NUMERICAL

Numerical Realization


- Sagemath
- Dimensionless Chua Eqs.
- Finite difference method
- Timestep = 0.000001
- Iterations = 100000
- Discarded (transients)= 10%
- Initial Conditions= Aleatory negative initial conditions (-10 to 0)




4

RESULTS

Numerical VS Experimental

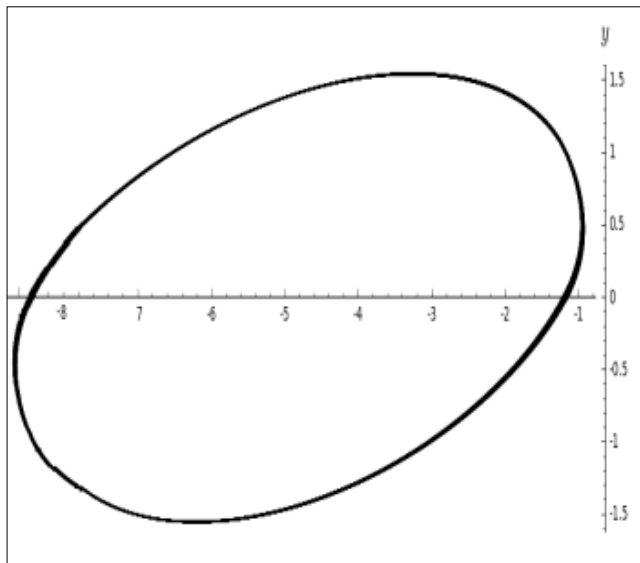


$R = 2015 \text{ } [\Omega]$

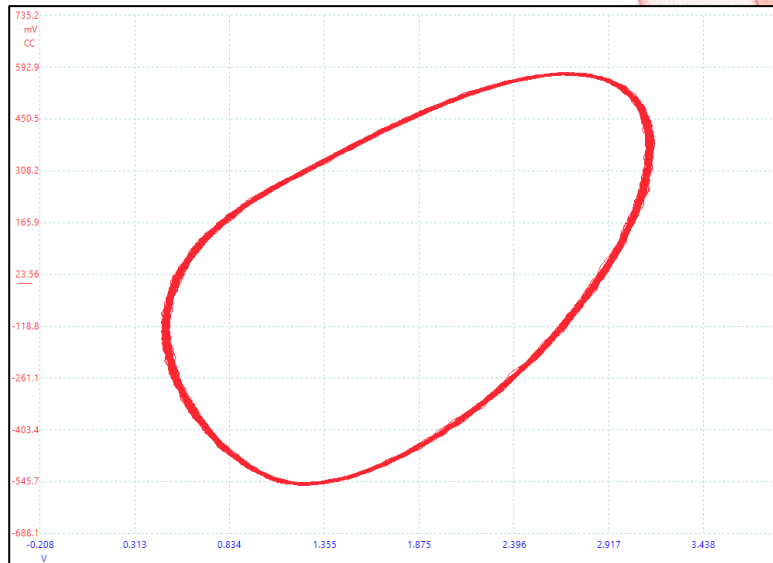


$R = 1777 \text{ } [\Omega]$

$\Delta = 11.81\%$

Numerical VS Experimental

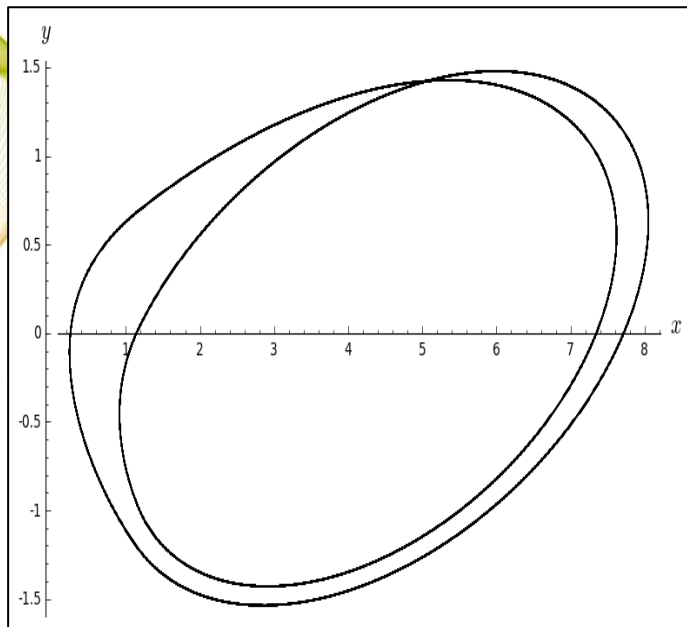


$R = 2001 [\Omega]$

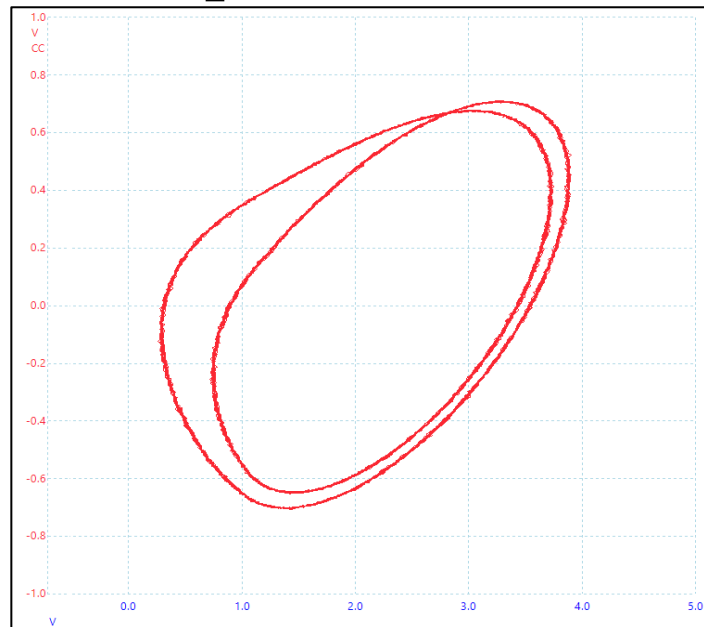


$R = 1714 [\Omega]$

$\Delta = 14.34\%$

Numerical VS Experimental

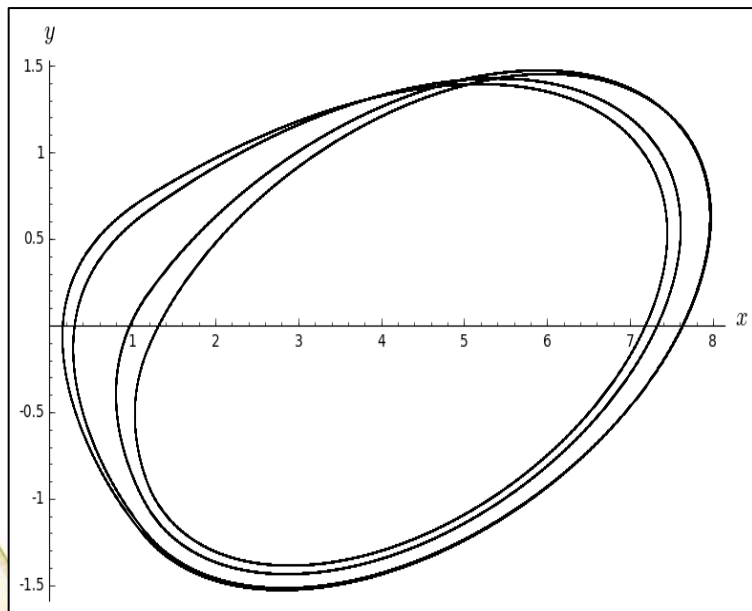


$R = 1998 [\Omega]$

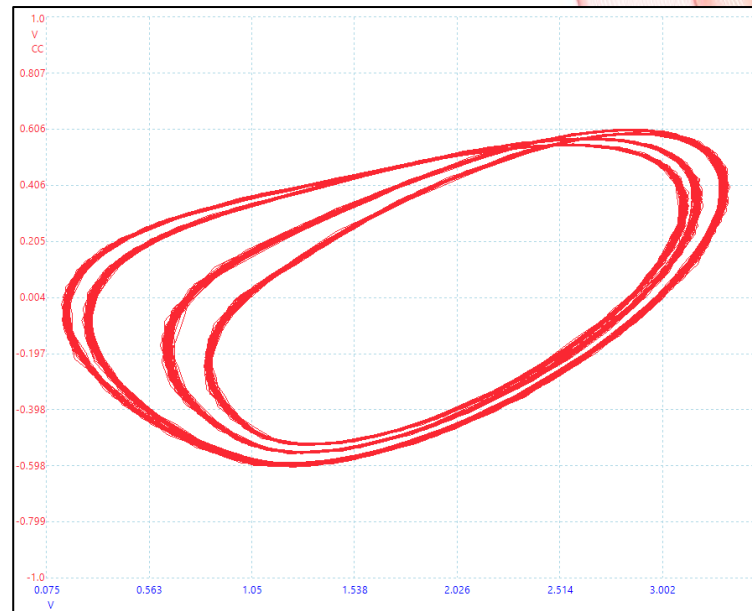


$R = 1701 [\Omega]$

$\Delta = 14.86\%$

Numerical VS Experimental

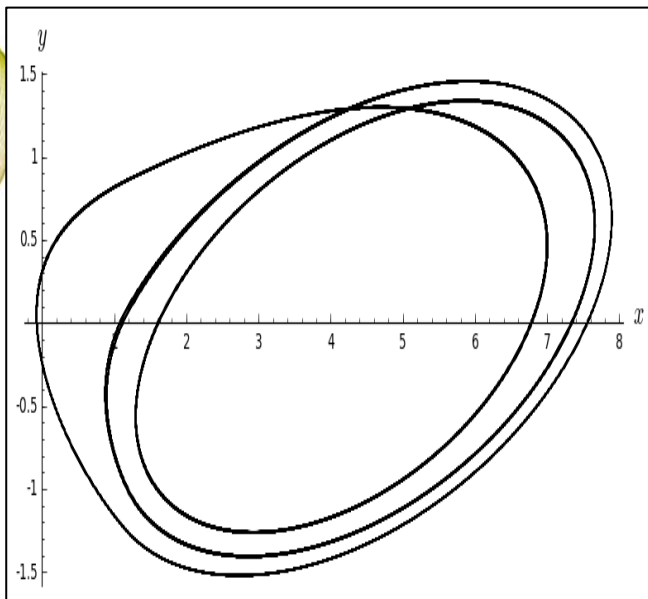


$R = 1993 \text{ } [\Omega]$

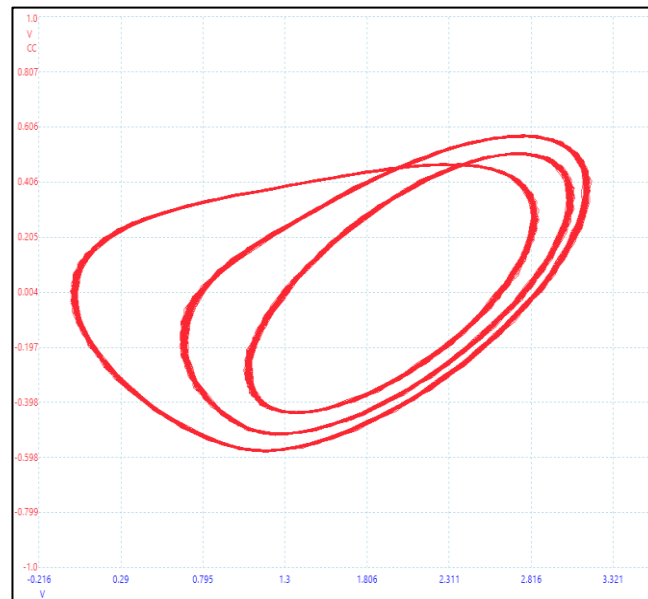


$R = 1677 \text{ } [\Omega]$

$\Delta = 15.85\%$

Numerical VS Experimental

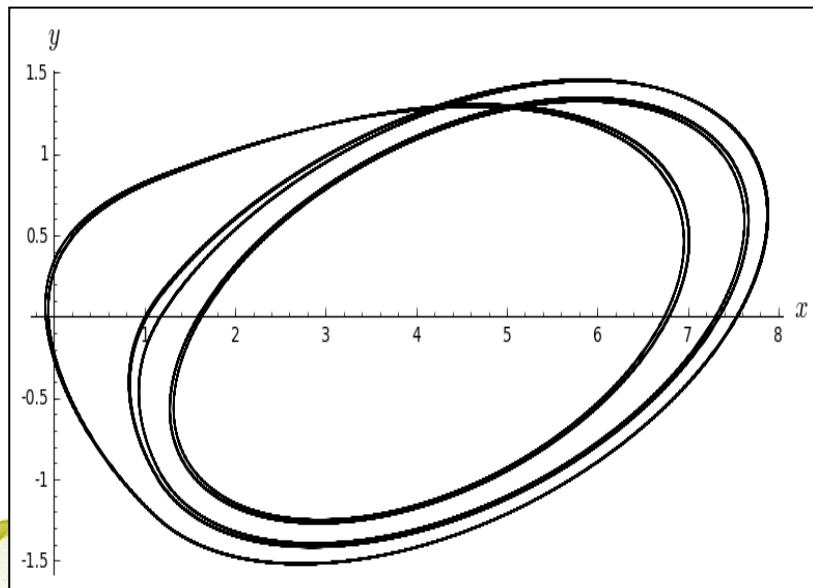


$R = 1992 [\Omega]$

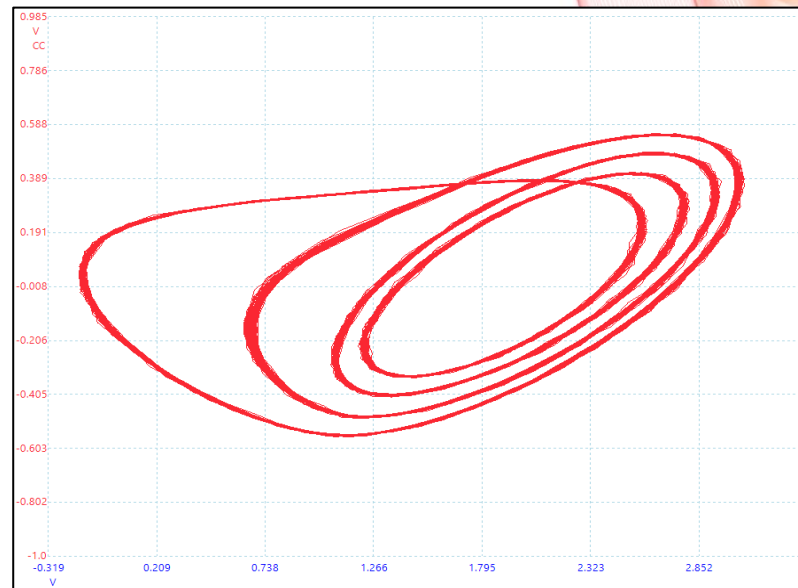


$R = 1669 [\Omega]$

$\Delta = 16.21\%$

Numerical VS Experimental

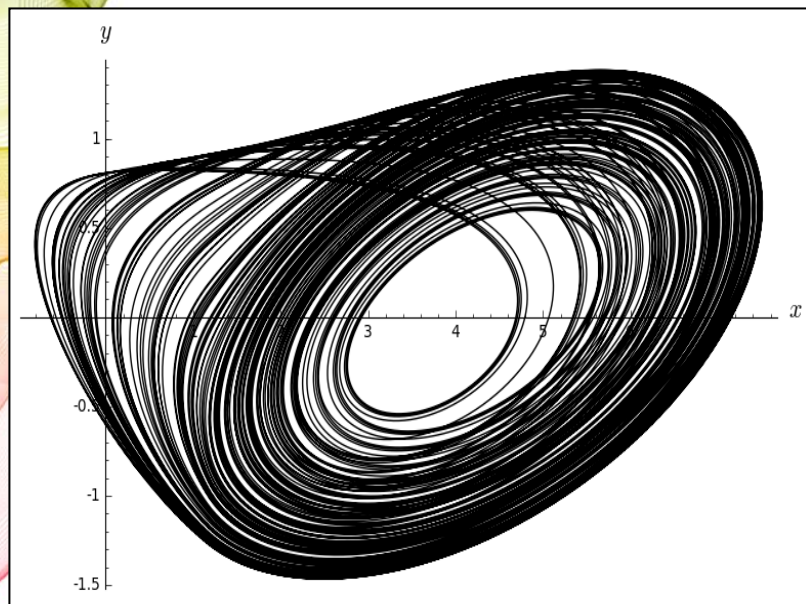


$R = 1974 [\Omega]$

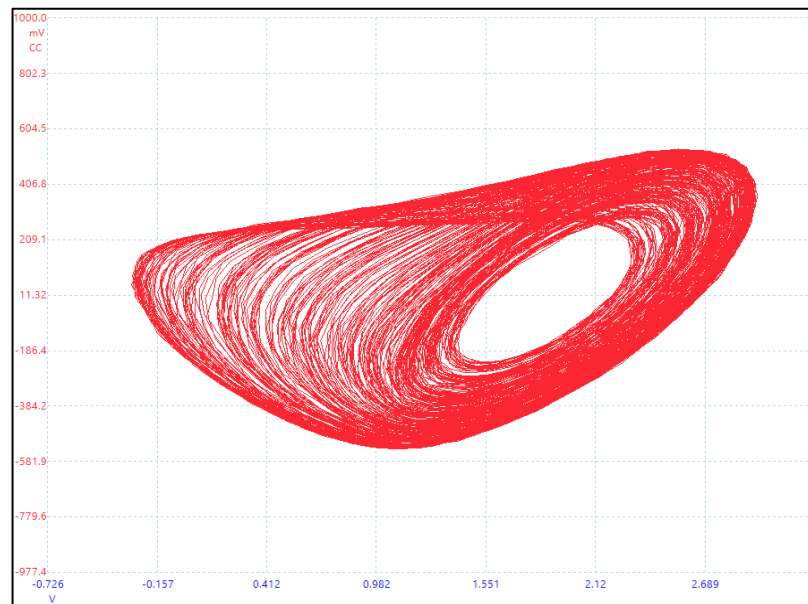


$R = 1650 [\Omega]$

$\Delta = 16.41\%$

Numerical VS Experimental

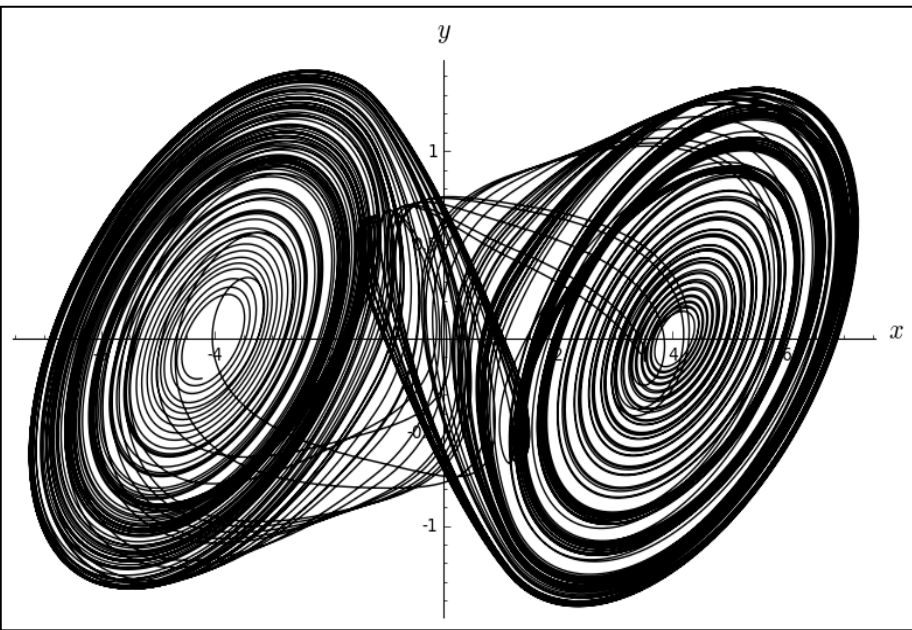


$$R = 1961 \, [\Omega]$$

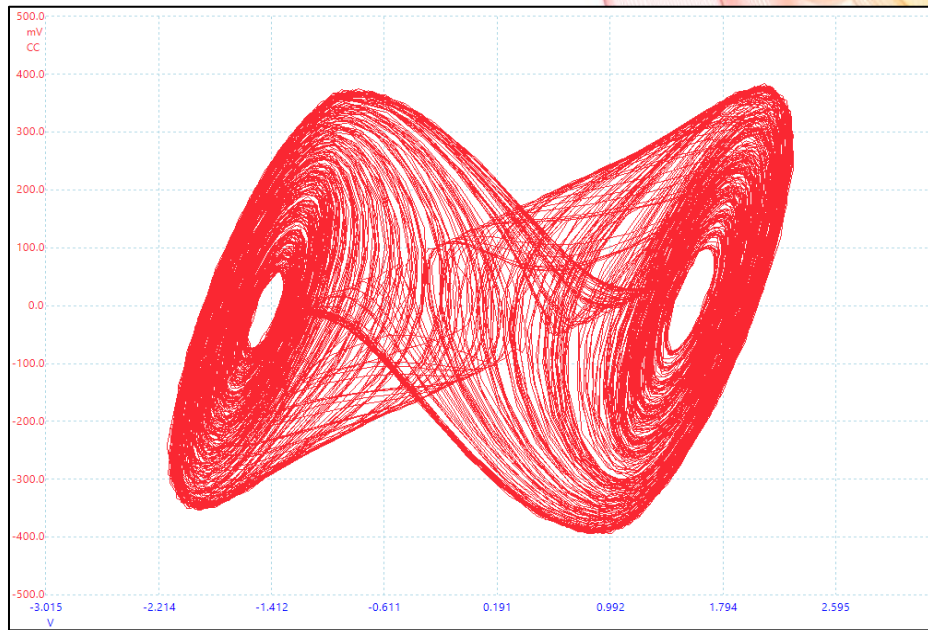


$$R = 1627 \, [\Omega]$$

$$\Delta = 17.03\%$$

Numerical VS Experimental

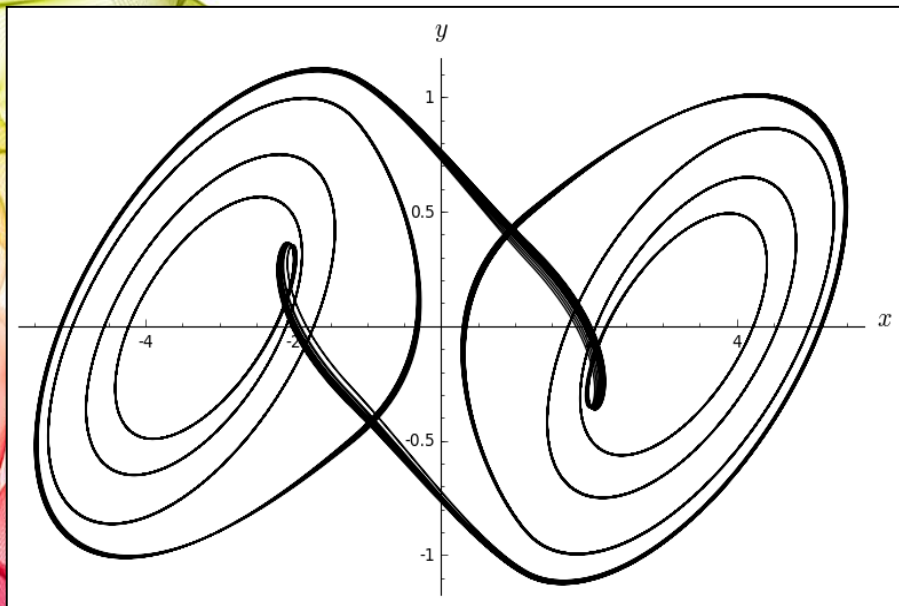

$R = 1955 [\Omega]$

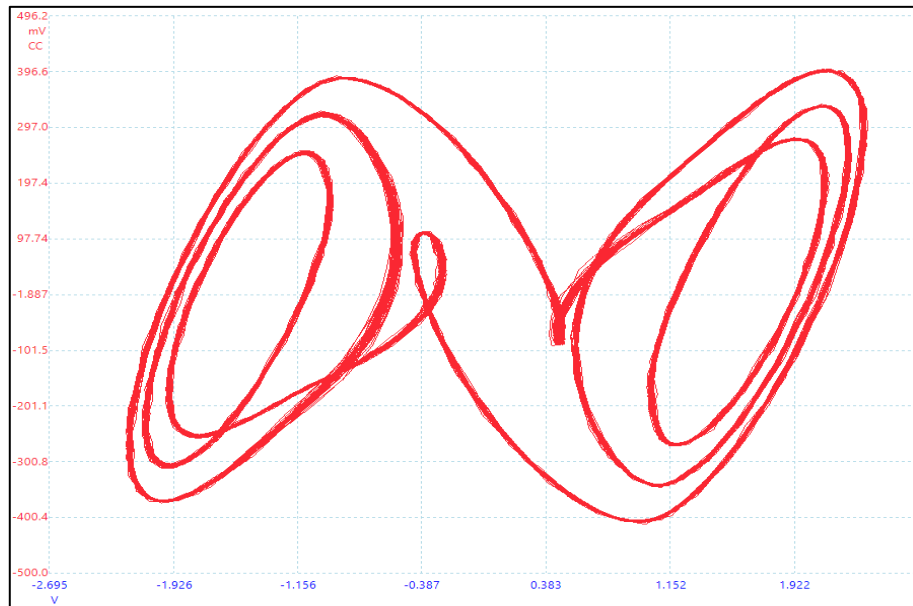


$R = 1614 [\Omega]$


(Not the same limit cycle ...)

$\Delta = 17.44\%$

Numerical VS Experimental

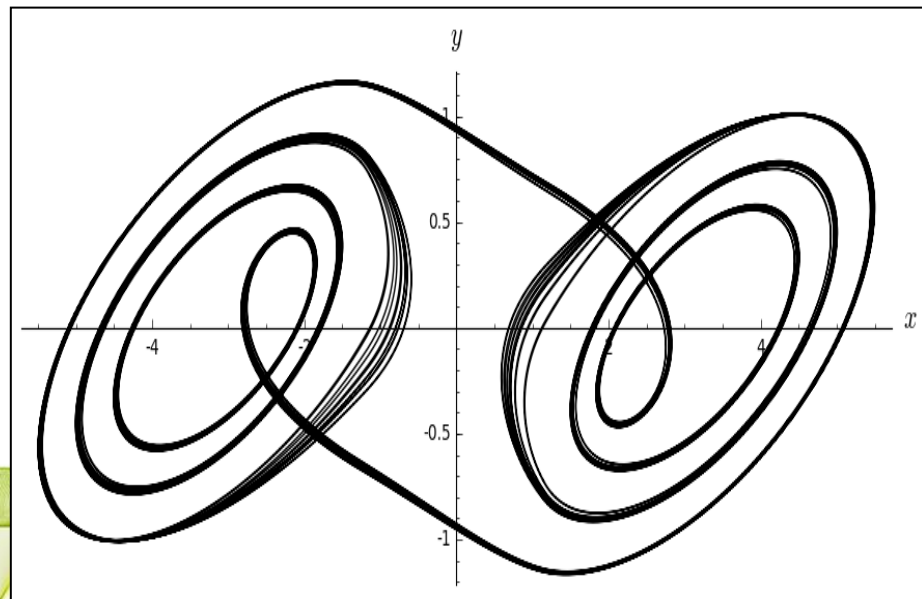


$R = 1851 \text{ } [\Omega]$

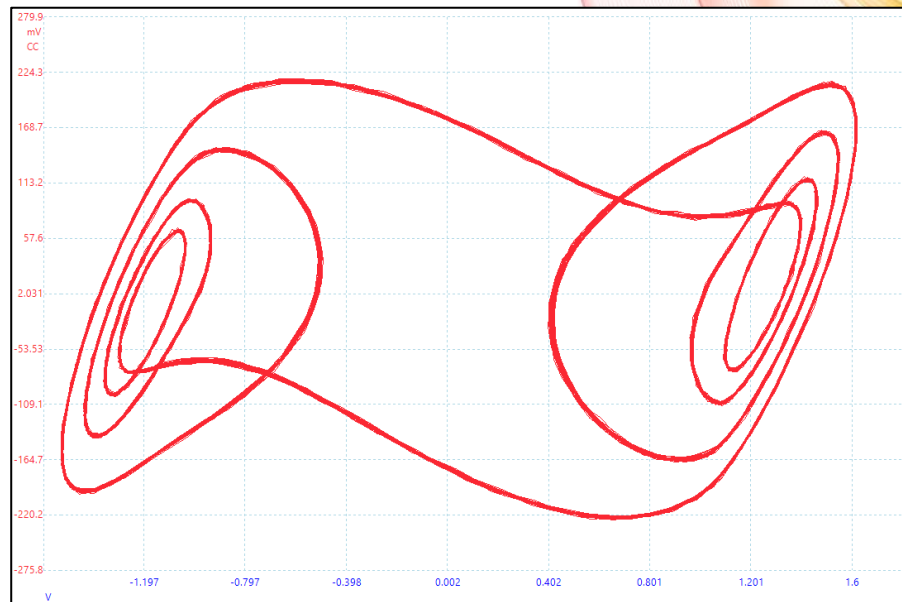


$R = 1607 \text{ } [\Omega]$

$\Delta = 13.18\%$

Numerical VS Experimental

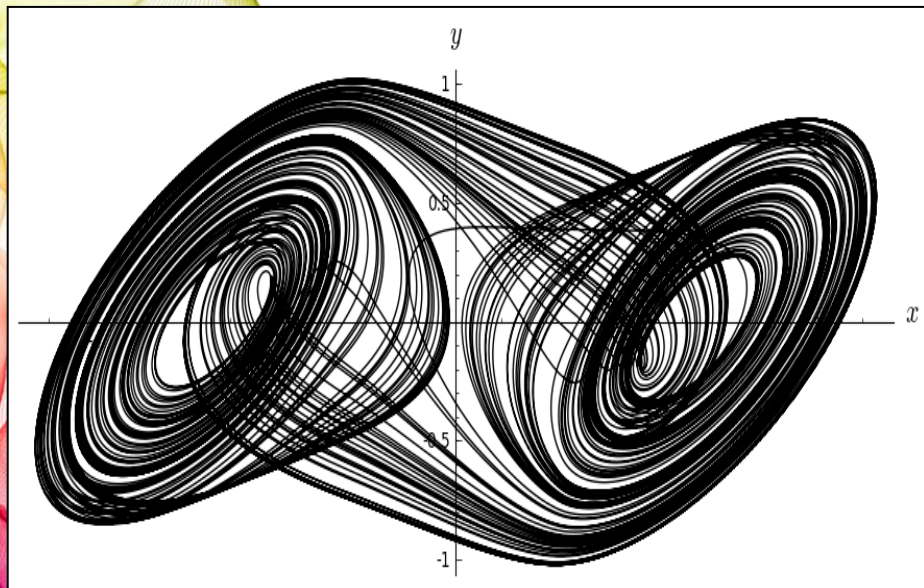


$$R = 1783 \text{ } [\Omega]$$

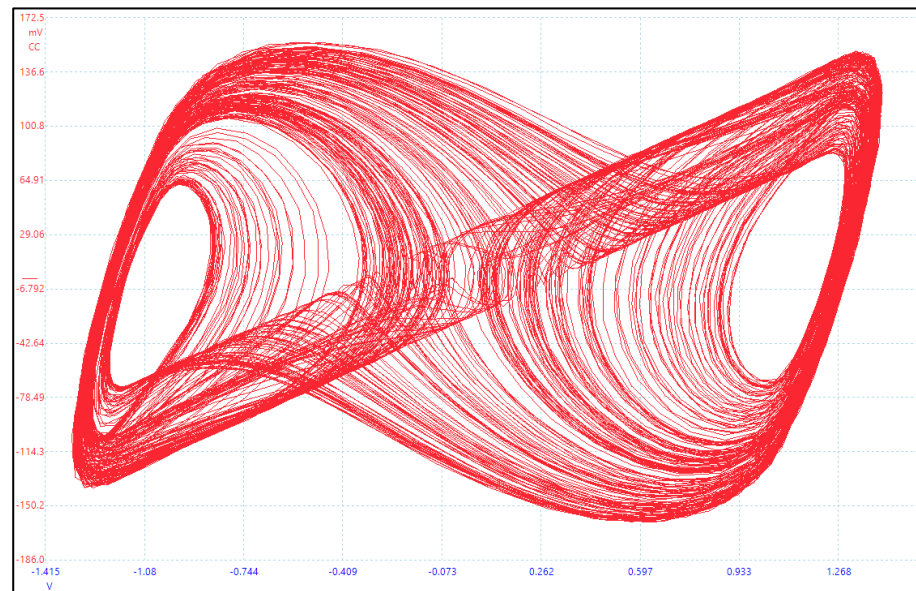

$$R = 1532 \text{ } [\Omega]$$

$$\Delta = 14.07\%$$

Numerical VS Experimental

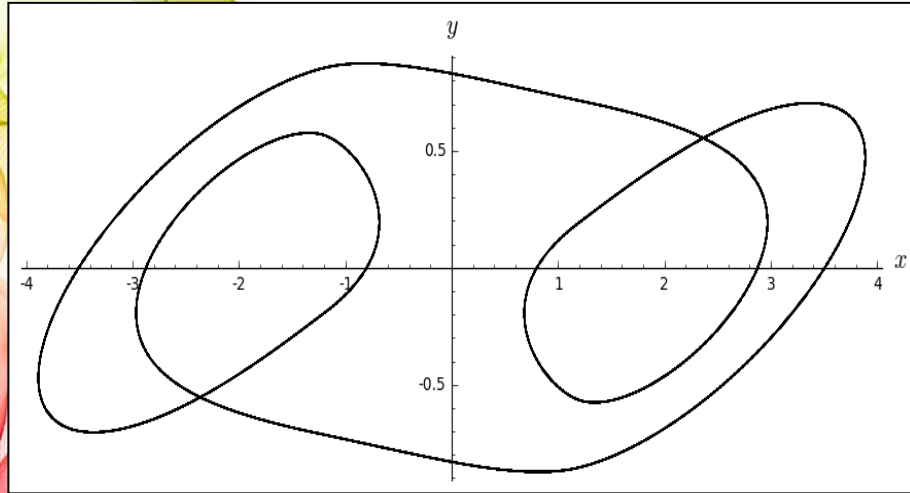


$$R = 1706 \, [\Omega]$$



$$R = 1427 \, [\Omega]$$


$$\Delta = 16.35\%$$

Numerical VS Experimental

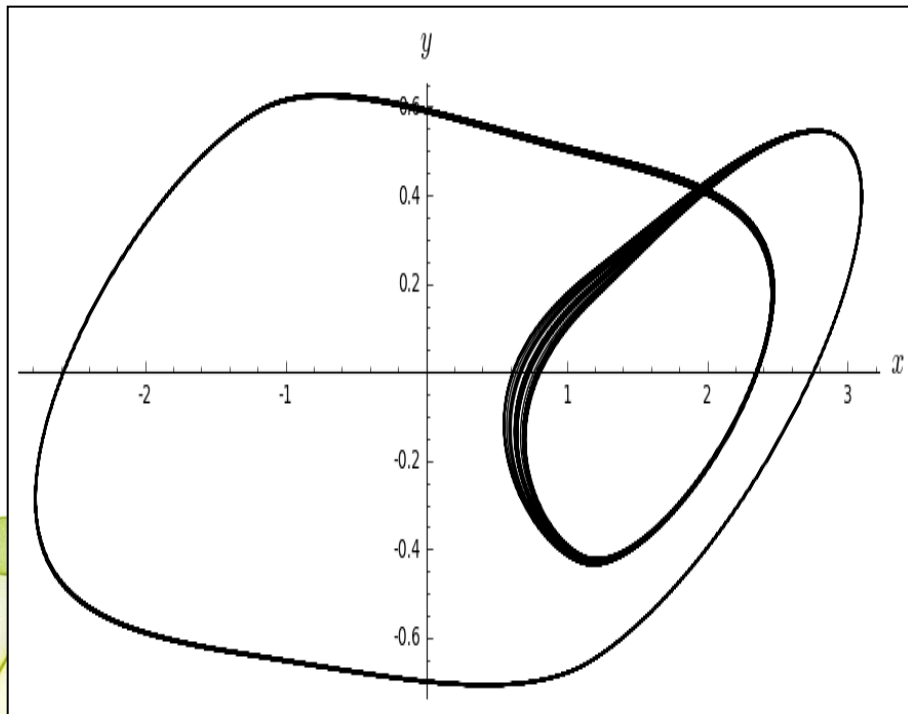



$$R = 1610 \text{ } [\Omega]$$

$$\Delta = 18.81\%$$

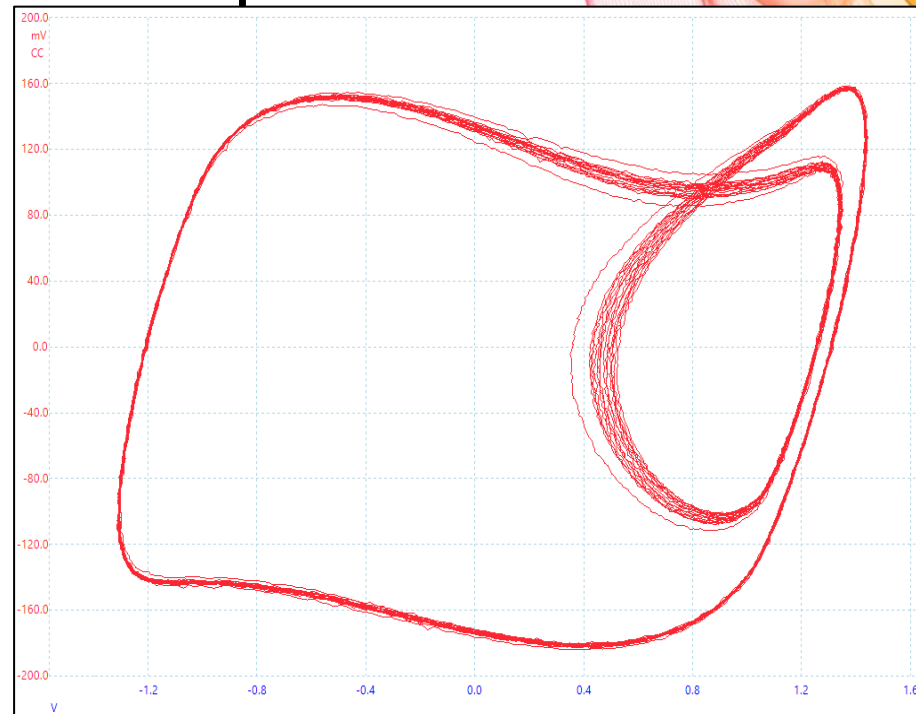



$$R = 1307 \text{ } [\Omega]$$

Numerical VS Experimental

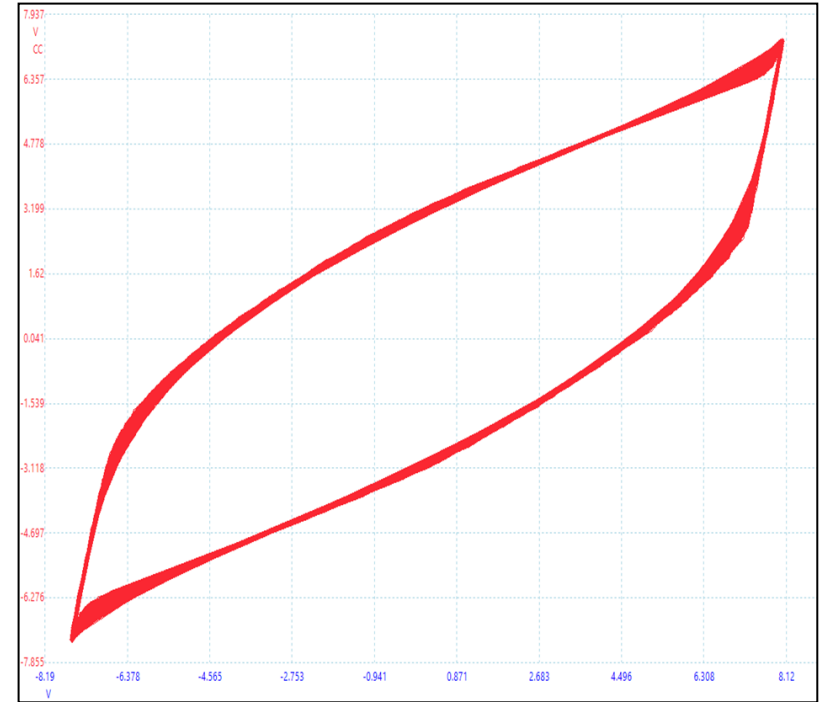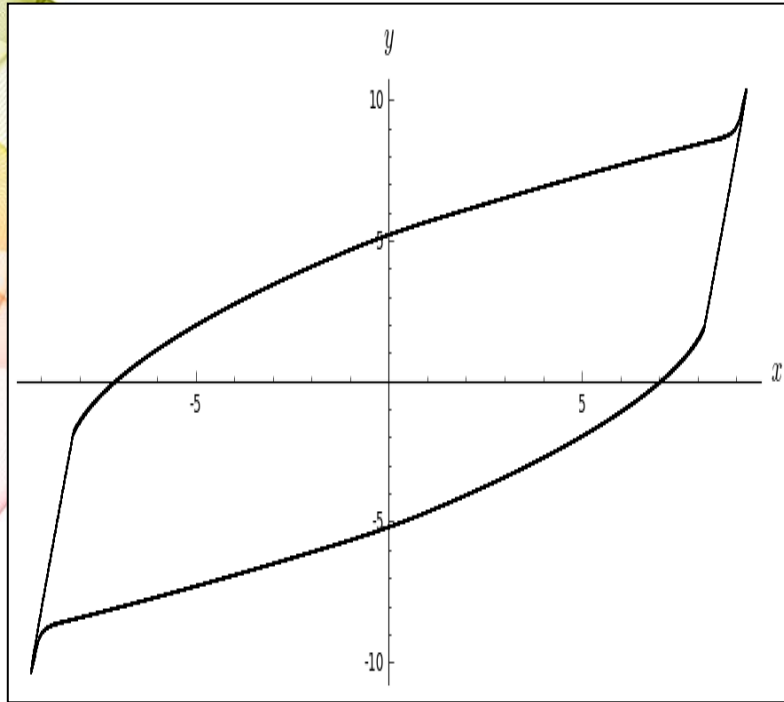

The outmost limit cycle

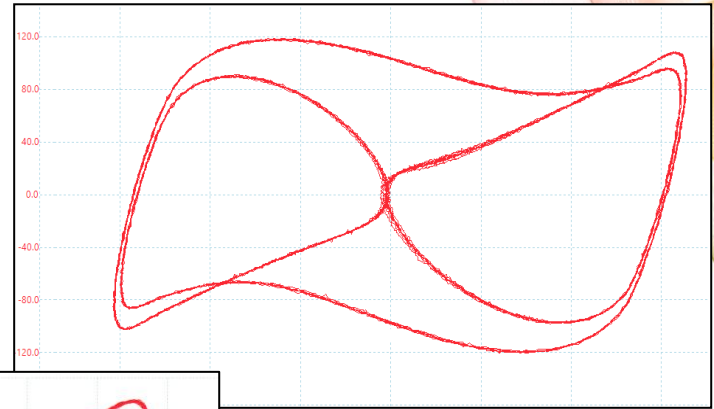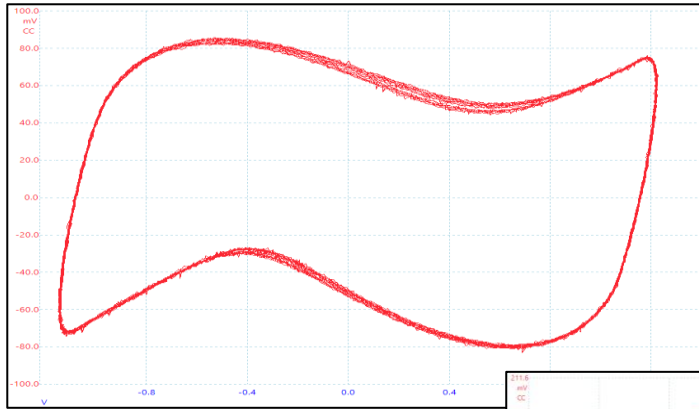
Experimental: Dancing around the outmost limit cycle



5

Synchronization


Bidirectional Chua's Circuit

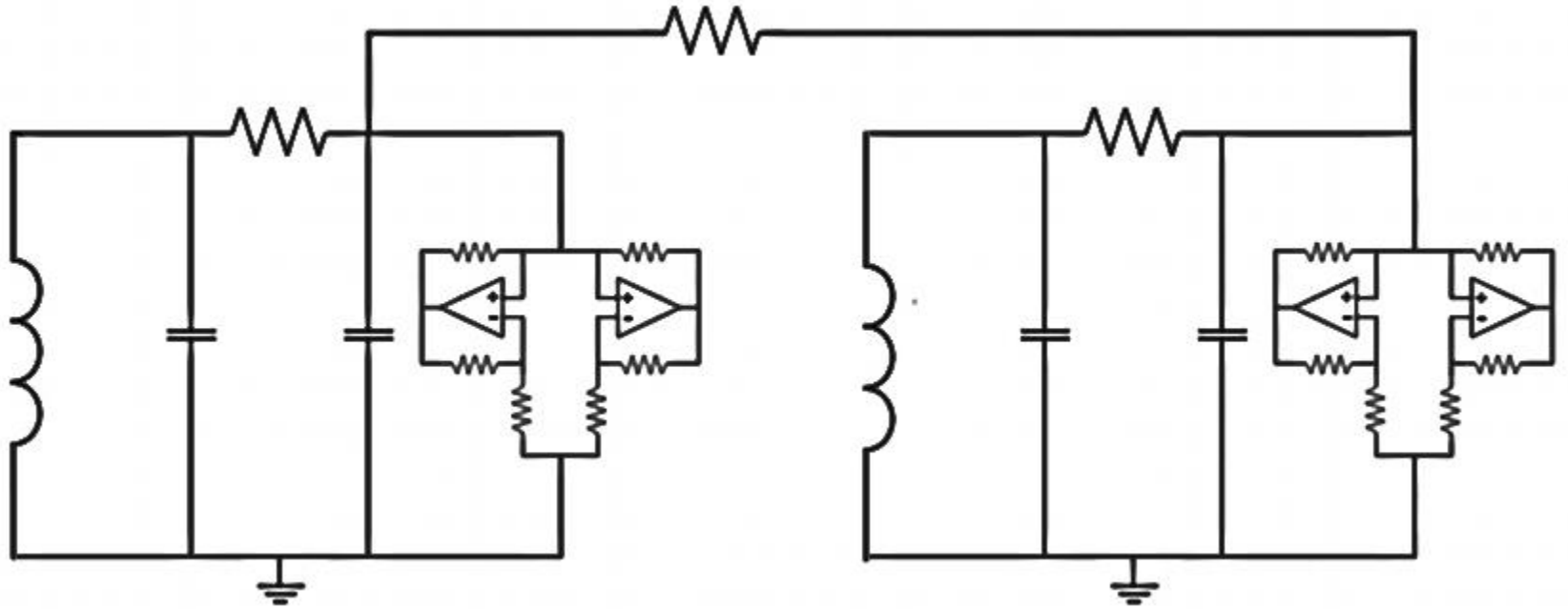

Experimental Realization





Chua 1

Chua 2




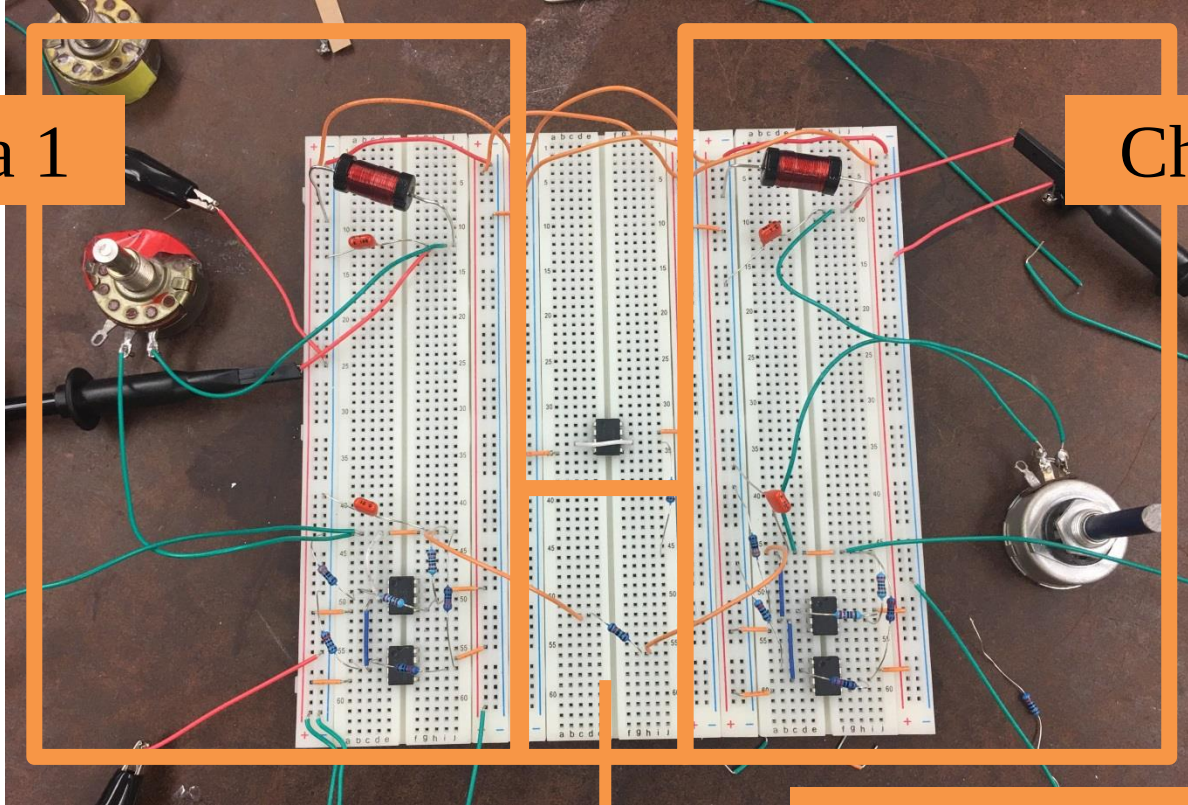


Synchronization Resistor

Bidirectional Chua's Circuit

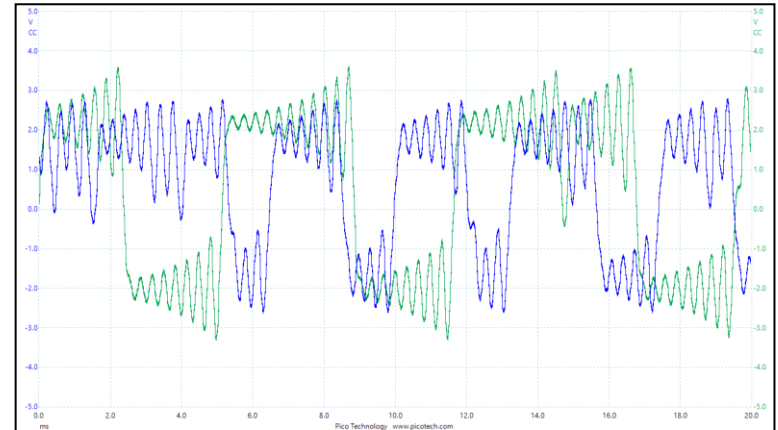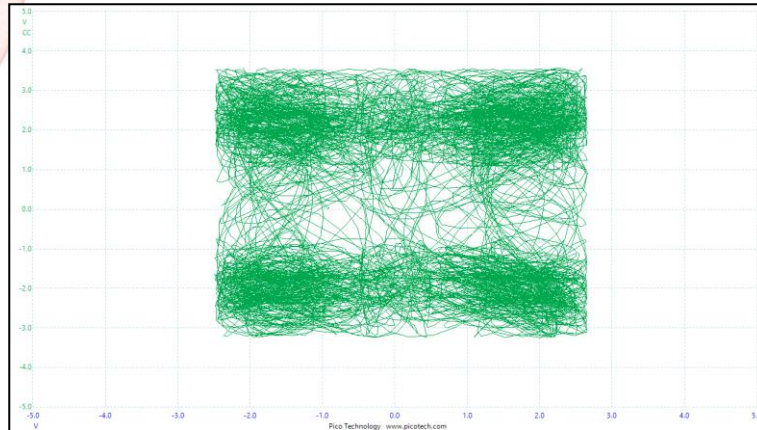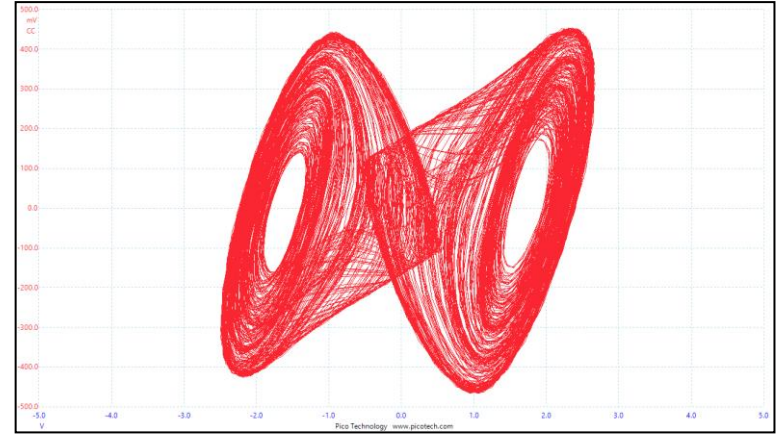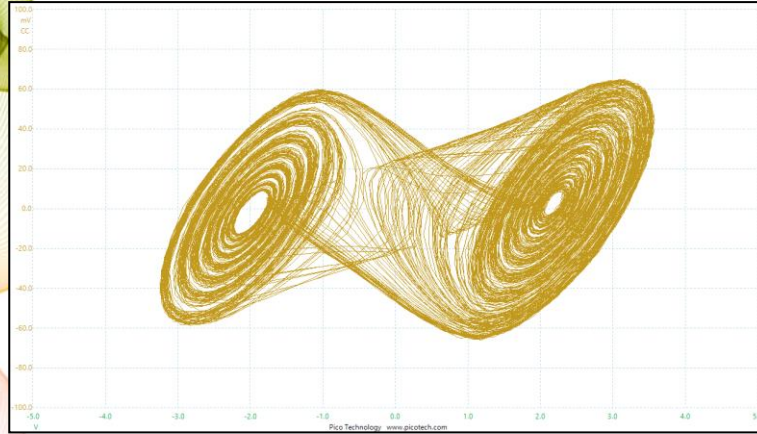

Bidirectional Chua's Circuit

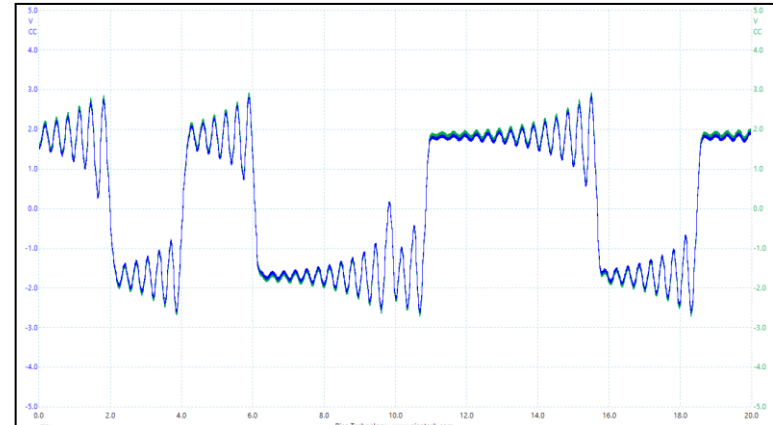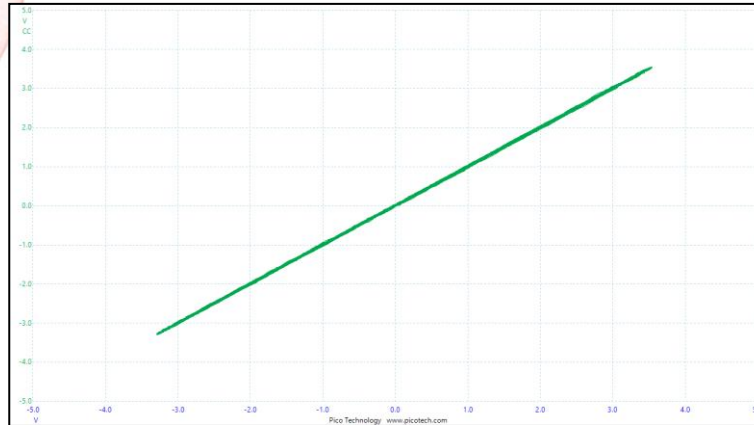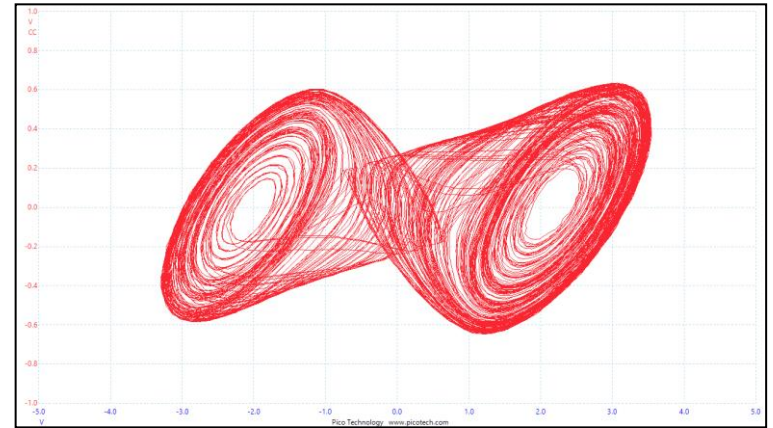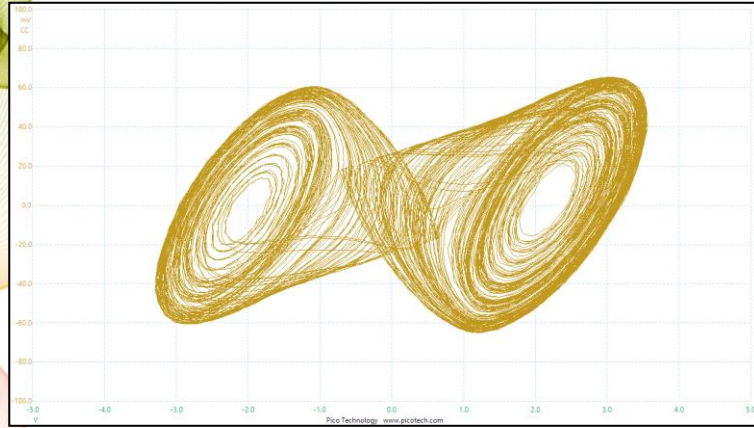

List of Sources

- [1] E. Lorenz, *The essence of chaos*. Seattle: University of Washington Press, 1995.
- [2] L. O. Chua, "Chua's circuit 10 years later," *International Journal of Circuit Theory and Applications*, vol. 22, no. 4, pp. 279–305, 1994.
- [3] Jakob Lavröd, "The Anatomy of a Chua Circuit", *Bachelor Thesis Equivalent to 15 ECTS*. Division of Mathematical Physics. Lunds Universitet.
- [4] K. G. Andersson and L.-C. Böiers, *Ordinära differentialekvationer / Karl Gustav Andersson, Lars-Christer Böiers*. Lund : Studentlitteratur, 1992 ; (Lund : Studentlitteratur), 1992.
- [5] G. Baker, *Chaotic dynamics : an introduction*. Cambridge New York: Cambridge University Press, 1996.
- [6] R. van der Steen, *Numerical and experimental analysis of multiple Chua circuits*. Eindhoven University of Technology, 2006.
- [7] Leonov, G.A., D.V. Ponomarenko and V.B. Smirnova, *Frequency methods for nonlinear analysis*. Theory and applications. World Scientific. Singapore, 1996.
- [8] M. P. Kennedy, "Robust op amp realization of chua's circuit," *Frequenz*, vol. 46, pp. 66–80, 1992.
- [9] Pecora, L.M. and T.L. Carroll, *Synchronization in chaotic systems*. Physical Review Letters 64(8), 821–824. 1990.
- [10] Dedieu, H., M.P. Kennedy and M. Hasler, *Chaos shift keying: Modulation and demodulation of a chaotic carrier using self-synchronizing Chua's circuits*. IEEE Transactions on Circuits and Systems II 40(10), 634–642. 1993.
- [11] Heagy, J.F., T.L. Carroll and L.M. Pecora. *Synchronous chaos in coupled oscillator systems*. Physical Review E 50(3), 1874–1886. 1994
- [12] Christine A. Skarda & Walter J. Freeman. *How brains make chaos in order to make sense of the world*. Behavioral and Brain Sciences 10. 1987
- [13] Garfinkel A. *A mathematics for physiology*. Am J Physiol. 1983